## 國立成功大學 111學年度碩士班招生考試試題

編 號: 156

系 所: 生物醫學工程學系

科 目:電子學

日 期: 0219

節 次:第2節

備 註:可使用計算機

## 國立成功大學 111 學年度碩士班招生考試試題

系 所:生物醫學工程學系

考試科目:電子學

考試日期:0219,節次:2

## 第1頁,共2頁

編號: 156


※ 考生請注意:本試題可使用計算機。 請於答案卷(卡)作答,於本試題紙上作答者,不予計分。

- (Total 20%) Please explain in what kind of conditions that the MOSFET enters saturation region / triode region (10%) and what are the drain current (ID) of NMOS in saturation / triode region (10%)?
- (Total 20%) (A) Please derive the Boolean function between output (Y) and input (A and B) as shown in
  the truth table of Table 1 (5%). Please draw the circuit using (B) Diode (5%), (C) BJT (5%), (D) MOSFET
  (5%) that can fulfill the Boolean function as you derive in (A).

Table 1

A (Input-1)	B (Input-2)	Y (Output)
0	0	0
0	1	1
1	1	0
1	0	1

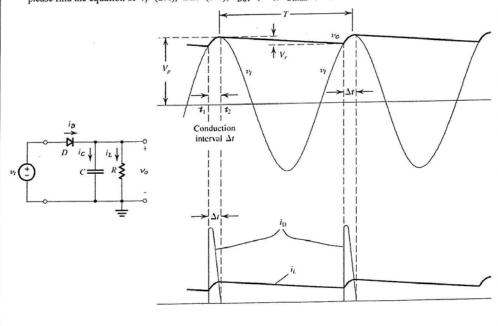(Total 10%) For the half-wave rectifier shown in the following figure (left), its corresponding input/output waveform is shown in the right side of the following figure. Let's assume the diode in the rectifier circuits is ideal, please find the equation of V<sub>r</sub> (2%), ωΔt (2%), i<sub>Dav</sub> (3%), i<sub>Dmax</sub> (3%).



國立成功大學 111 學年度碩士班招生考試試題

編號: 156


所:生物醫學工程學系

考試科目:電子學

考試日期:0219,節次:2
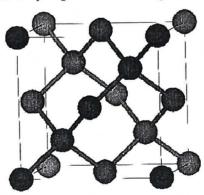
## 第2頁,共2頁

- (Total 20%) (A) Please draw the circuit of BJT differential amplifier with BJT current-mirror loads (5%) and drive (B) differential gain (5%), (C) input differential resistance (5%), and (D) systematic input offset voltage (5%).
- 5. (Total 20%) Please draw the circuit of common-base amplifier (5%) and find its output resistance (15%).
- 6. (Total 10%) The lattice structure of Germanium is the same as silicon (diamond sturcture), the atomic weight Germanium is 72.59, and the lattice constant is 0.564 nm. Find the density (g/cm³) (4%), atomic density (atoms/cm³) (3%), and the spacing between nearest-neighbor atoms in Germanium (3%).



Lattice structure of Germanium