

國立成功大學  
114學年度碩士班招生考試試題

編 號：119

系 所：生物醫學工程學系

科 目：電子學

日 期：0210

節 次：第 2 節

注 意：1. 可使用計算機  
2. 請於答案卷(卡)作答，於  
試題上作答，不予計分。

**Question 1: Semiconductor Fundamentals (5 points)**

- a. Explain what a semiconductor is and its basic properties. (2 points)
- b. Describe the differences between p-type and n-type semiconductors. Include their doping processes and charge carriers. (3 points)

**Question 2: Formation of a PN Junction (3 points)**

Explain the process of creating a PN junction. Use diagrams to illustrate how p-type and n-type materials form a depletion region and the resulting electric field.

**Question 3: Bipolar Junction Transistor (BJT) (5 points)**

- a. Describe the structure of a BJT. (2 points)
- b. Explain the principle of operation for the BJT, focusing on the active mode. (3 points)

**Question 4: Metal-Oxide-Semiconductor Field-Effect Transistor (MOSFET) (7 points)**

- a. Explain the structure of a MOSFET, emphasizing the role of the gate, source, and drain. (3 points)
- b. Discuss the different operating regions of a MOSFET (cut-off, linear/triode, and saturation regions) and their significance. (4 points)

**Question 5: Common Base Amplifier (20 points)**

- a. Circuit Diagram: Draw the circuit diagram of a Common Base (CB) amplifier. Clearly label the input, output, and biasing components. (3 points)
- b. Characteristics and Applications:
  - i. Explain the key characteristics of a CB amplifier, including input impedance, output impedance, and voltage gain. (3 points)
  - ii. Discuss two practical applications of CB amplifiers. (2 points)
- c. Analysis and Derivations:
  - i. Derive the voltage gain equation for a CB amplifier. (4 points)
  - ii. Derive the input resistance/output resistance of a CB amplifier, showing all steps. (4 points)
- d. Frequency Response:
  - i. Explain the low-frequency, mid-frequency, and high-frequency behavior of a CB amplifier. (2 points)
  - ii. Discuss how the bypass capacitor (if present) impacts the frequency response. (2 points)

**Question 6: Current-Mirror Loaded MOS Differential Amplifier (20 points)**

- a. Circuit Diagram:

Draw the circuit diagram of a current-mirror loaded MOS differential amplifier. Clearly label all key components, including the differential pair, current mirror, input nodes, and output nodes. (5 points)
- b. Common-Mode Gain:

Derive the expression for the common-mode gain  $A_{CM}$  of the amplifier. Include all necessary steps and assumptions in your derivation. (7 points)
- c. Common-Mode Rejection Ratio (CMRR):
  - i. Define the common-mode rejection ratio (CMRR) and explain its significance in differential amplifiers. (3 points)
  - ii. Derive the expression for the CMRR in terms of the differential gain  $A_{DM}$  and common-mode gain  $A_{CM}$ . Show all steps in the derivation. (5 points)

**Question 7: Operational Amplifiers in Biomedical Signal Applications (20 points)**

Operational amplifiers (OPAs) are widely used in biomedical signal processing due to their versatility and precision. Answer the following questions based on their applications:

**a. Characteristics and Requirements:**

Discuss the essential characteristics of an operational amplifier that make it suitable for biomedical applications. Consider parameters such as input impedance, output impedance, gain, and noise performance. (5 points)

**b. Applications in Biomedical Signals:**

- Explain how OPAs are used in amplifying weak biomedical signals, such as ECG or EEG signals. Include a discussion on the role of differential amplification in rejecting noise. (5 points)
- Describe the role of an instrumentation amplifier (which uses OPAs) in biomedical circuits and why it is preferred for precise signal acquisition. (5 points)

**c. Practical Design Considerations:**

Discuss two challenges encountered when designing OPA-based circuits for biomedical applications and propose solutions to address them. (5 points)

**Question 8: Please answer the following questions (20 points)****a. DC bias design**

Perform a DC bias design for the amplifier in Figure 1. For this purpose, assume  $\beta$  is very high and  $V_{BE} = 0.7\text{ V}$ , and neglect the Early effect. Design to obtain a DC base voltage of  $V_{CC}/3$ , a DC emitter current of 1 mA, and a DC voltage at the collector that allows for  $\pm 1\text{ V}$  signal swing at the collector with the minimum collector voltage no lower than  $V_B$ . Use a DC current in the base voltage divider is  $I_E/10$ . What values are required for  $R_{B1}$ ,  $R_{B2}$ ,  $R_E$ , and  $R_C$ ? (4 points)

**b. Voltage and current calculation**

If the transistor has  $\beta = 100$ , find the actual values obtained for  $I_E$ ,  $I_C$ ,  $V_B$ , and  $V_C$ . (4 points)

**c. Small signal parameters**

What are the values of  $g_m$ ,  $r_e$ , and  $r_{\pi}$  at the DC bias point? (2 points)

**d. Biasing resistor design**

Assuming very large coupling and bypass capacitors, find the values of  $R_{E1}$  and  $R_{E2}$  that result in  $R_{in} = 10\text{ k}\Omega$ . (4 points)

**e. Overall voltage gain**

Find the overall voltage gain  $G_v = \frac{v_o}{v_{sig}}$ . (6 points)

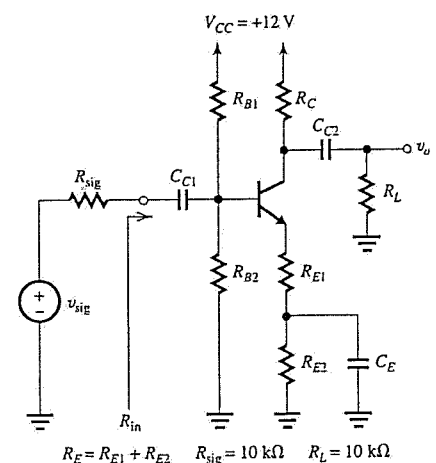


Figure 1.