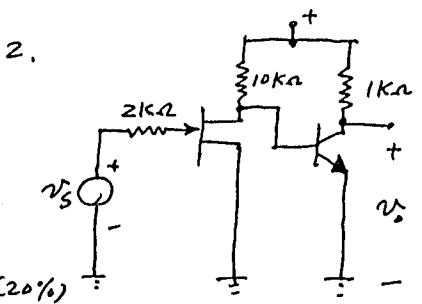



For the current mirror shown, the transistors Q_1 & Q_2 are identical. (a) Determine I_C in terms of circuit parameters (b) Evaluate I_C for $V_{CC} = 10V$, $R = 10K\Omega$ and $\beta_F = 100$. (c) Repeat (b) for $\beta_F = 200$. (4) Explain why this circuit is called "current mirror". (5) Explain why I_C is a constant current.




The JFET in the circuit shown has $g_m = 2mS$, $r_d = 30K\Omega$, $C_{gs} = 10pF$, $C_{gd} = 5pF$ and $C_{ds} = 5pF$. The BJT parameters are: $r_{\pi} = 2.5K\Omega$, $\beta_0 = 125$, $C_{\pi} = 100pF$, and $C_{\mu} = 1.5pF$.

(a) Determine A_{vo} and the approximate value of f_H .

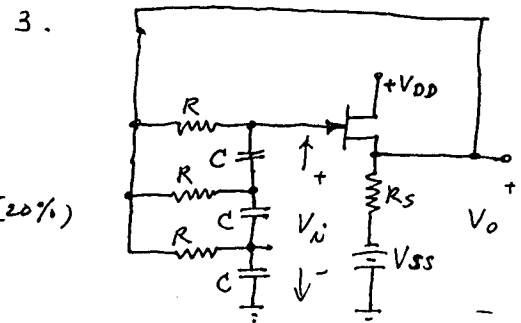(b) Estimate the frequency of the nearest nondominant pole.



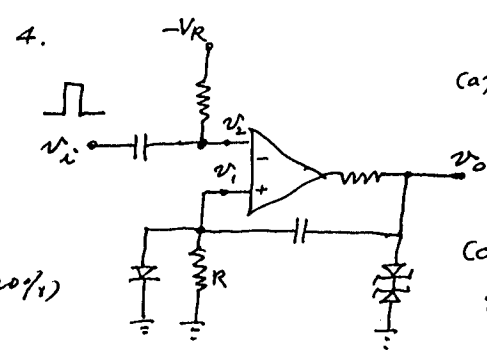For the circuit shown, find (a) The frequency of oscillation (b) the minimum gain of the source follower require for oscillations.




(a) For the circuit shown, find v_2 , v_0 and v_1 in the quiescent state.

(b) Verify that T is given by $T = RC \ln \frac{V_0}{V_R}$

(c) At $t=0$, a narrow, positive, triggering pulse v_i whose magnitude exceeds V_R is applied. At $t=0^+$, find v_0 and v_1 (Remember that the

voltage across a capacitor cannot change instantaneously) Now plot the waveform v_0 and v_1 as a function of time. Demonstrate that the circuit behaves as a monostable multivibrator with a pulse width T .

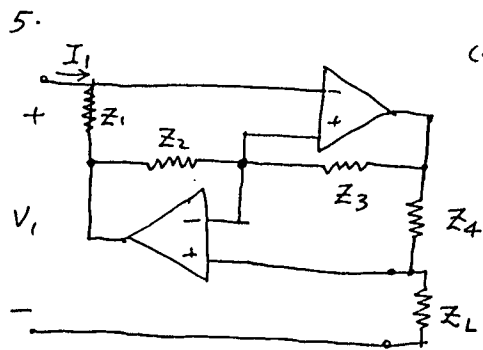(d) Find v_0 and v_1 at $t=T^+$ and continue the waveforms until the steady state is reached. What is the recovery-time constant?



(a) For the circuit shown (GIC), show that if the OP-Amps are ideal, then $Y_i = \frac{I_1}{V_1} = \frac{Y_1 Y_3}{Y_2 Y_4} Y_L$

(b) The circuit is often used to simulate an inductance on a chip. Show that if $Y_4 = sC_4$ and all other components are resistive, Y_i is inductive.

(20%) (c) Assuming that any resistance can lie between 0.1 and $10\text{ k}\Omega$ and $10 \leq C \leq 500\text{ pF}$, what is the range of inductance values possible?