

- (1) In the circuit shown in Figure 1, the transistor used for Q1 and Q2 has the $\beta_F=200$. (15%)
- With $v_1=v_2=0$, determine the bias currents I_{CQ} and I_{BQ} , and the output voltages v_{o1} and v_{o2} .
 - Evaluate A_{DM} , A_{CM} , and the CMRR.
 - Determine R_{id} and R_{ic} .
 - Design a current mirror to replace the $14.3\text{-K}\Omega$ resistance to establish the same bias currents, and find the CMRR.

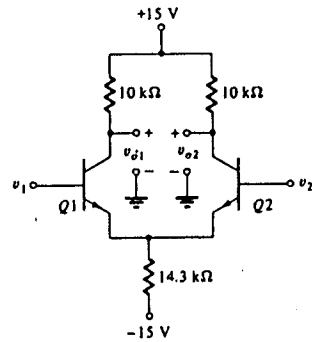


Figure 1

- (2) Figure 2 shows the general form of an oscillator circuit. (20%)
- Draw the equivalent circuit and determine the return ratio.
 - Draw the Colpitts oscillator, determine its oscillation frequency, and explain its operation.
 - Repeat (b) with the Hartley oscillator.

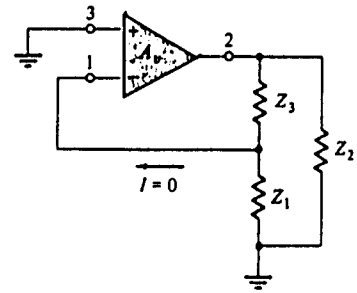


Figure 2

- (3) In the circuit shown in Figure 3, it is assumed that $R_D \gg r_{\pi}$, $r_d \gg r_{\pi}$, $\beta_o \gg 1$, and $\mu \gg 1$. (15%)
- Determine $A_{v1} = v_{o1}/v_s$.
 - Determine $A_{v2} = v_{o2}/v_s$.

- (4) Assuming that the op-amps in Figure 4 are all ideal, find the $Z_{in}(j\omega)$. (15%)

- (5) (15%)
- Draw the block diagram of a successive approximation type of analog-to-digital (A/D) converter. Explain the operation principle.
 - Compare four different types of A/D, successive approximation, integrating, flash, and V/F counting converters, in speed, resolution, noise immunity, and cost.

- (6) Figure 5 shows the circuit of a low-pass Butterworth filter. (20%)

- Determine the v_o/v_i .
- Explain the aliasing phenomenon during data sampling.
- Assuming that a bio-signal with frequency bandwidth 0-200 Hz, choose the appropriate sampling rate. Utilize the Butterworth filter, shown in Figure 5, to design an anti-aliasing filter. ($R=100\text{ K}\Omega$)

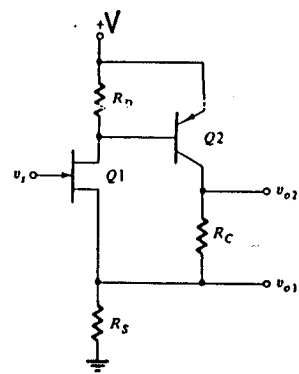


Figure 3

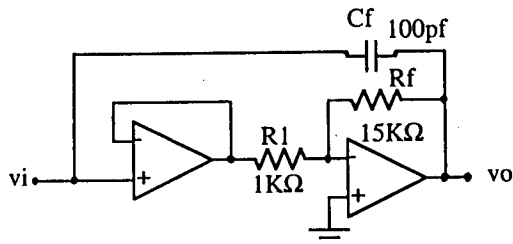


Figure 4

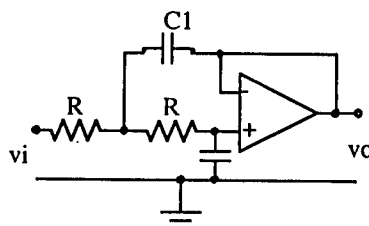


Figure 5