

- Describe the following terms used in operational amplifier: (a) compensation capacitor; (b) slew rate; (c) CMRR; (d) offset voltage; (e) gain-bandwidth product. (15%)
- Design a band-pass active filter with pass band frequencies of 10 - 100 Hz, and draw the circuit and derive the values for the R and C elements. (15%)
- Use the NOR gates to realize (a) NOT gate (b) RS flip-flop (c) D-type flip-flop. Give the truth tables for (b) and (c). (20%)
- For the circuit as shown in Figure 1, find the frequency of oscillation and the minimum value of R. (15%)
- A CS-CS cascade uses identical JFETs whose parameters are: $g_m=1$ mS, $R_d=40$ k Ω , $C_{gs}=5$ pF, $C_{gd}=1$ pF, and $C_{ds}=1$ pF. (a) With $R_s=5$ k Ω , $R_{D1}=40$ k Ω , and $R_{D2}=10$ k Ω , determine A_{vo} and the approximate value of f_H . (b) Estimate the frequency of the nearest nondominant pole. (20%)
- For a circuit with $v_i(t)$ as shown in Figure 2, the transistor has $\beta_F=100$ and negligible reverse saturation current. The input voltage v_i in the circuit is $v_i(t)=2.0+1.0\sin 2\pi 10^3 t$. Sketch $v_o(t)$ for one cycle. (15%)

Figure 1

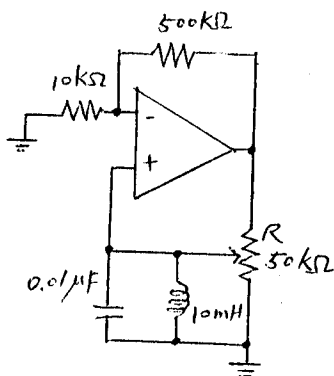


Figure 2

