

1. (15 %) Describe the following terms. (a) Schottky barrier diode, (b) Tunneling current, (c) phototransistor.
2. (20 %) Design a base-bias amplifier with four resistors ( $R_1$ ,  $R_2$ ,  $R_C$ , and  $R_E$ ), a *npn* transistor ( $Q_1$ ), and a 12 V d.c. voltage source. Draw your circuit. Determine the  $I_c$  and  $V_{CE}$  for your circuit if the transistor has  $\beta_F$ .
3. (15 %) Draw an OP-Amp version of phase-shift oscillator. Determine the oscillation frequency.
4. (15 %) Please draw a circuit of an inverting half-wave perfect rectifier using OP-Amp, resistors, and diodes. Plot the input-output characteristics for the circuit output.
5. (20 %) For the security of a supermarket, please design a digital system to count the number of customers entering and leaving a single gate. (Hint: You may use the photodiode, standard logic circuit, or microprocessor, etc.)
6. (15 %) The isolation amplifier is a very important component in medical device. Please describe the general principles of isolation amplifier. Sketch two general approaches to achieve an isolation amplifier.