

- (15%) Describe the characteristics of the following terms:
 - Surface Mount Device (SMD);
 - Ball Grid Array (BGA);
 - Electronic Design Automation (EDA);
 - Flash memory;
 - Gallium-Arsenide (GaAs) digital circuits.

- (15%) For the PNP differential amplifier circuit (Fig.1), let $V_{CC} = 15V$, $R_C = 15 K\Omega$, $R_B = 10 K\Omega$, and $R_{EE} = 50 K\Omega$.

- Draw the equivalent circuit of the differential amplifier;
- Find the common mode gain and Derive the CMRR of the differential amplifier.

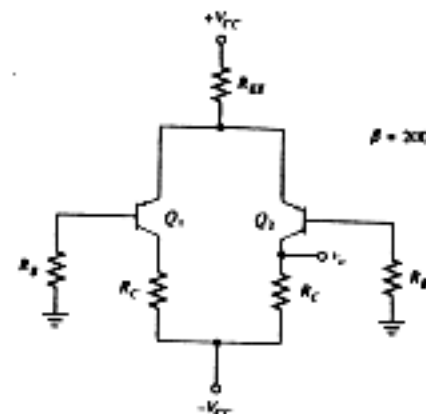


Fig. 1

- (20%) Assumed that the op-amps in Fig. 2 are ideal.

- Derive the transfer function of the high pass filter. You can solve the R-C network by assuming $V_+ = V_o$ and using KCL theorem.
- What is the high-frequency gain?
- Design the circuit for a maximally flat response with a 3-dB frequency of 1000 rad/s. By using $C_1 = C_2 = 10$ nF, please give the values for R_3 and R_4 . (Hint: The polynomial of the active filter is equal to $s^2 / (s^2 + s(\omega_0/Q) + \omega_0^2)$. For a maximally flat response, $Q = 1/\sqrt{2}$ and $\omega_{3dB} = \omega_0$.)

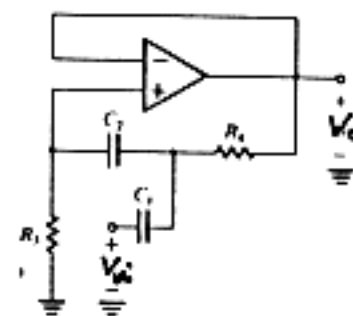


Fig. 2

- (20%) Fig. 3(b) shows a simple astable multivibrator circuit using CMOS gates. The finite output resistance of the CMOS gate can be neglected. Also, the diodes at the gate input are assumed ideal.

- Using the waveform V_{O1} in Fig. 3(a), please verify the period $T = CR \ln (V_{DD}^2 / (V_{DD}V_{th} - V_{th}^2))$. V_{th} denotes the threshold voltage.
- Plot the waveform in v_{i1} and label the V_{th} , V_{DD} , and T.
- Find suitable values for R and C to obtain oscillation $f_o = 72.1$ KHz.

- (15%) Please use a single type of digital gate (e.g. AND, OR, NAND, or NOR gates) to realize (a) RS flip-flop; (b) D-type flip-flop. Also, give their truth tables.

- (15%) A clinical neurologist in National Cheng Kung University Hospital wishes to set up a digital controlled constant current source for nerve stimulation. Assumed that the desired current is between 0 - 31 μA with an increment of 1 μA (i.e. current resolution). Please give your design by using D/A and constant current source.

- Draw your circuit design of the D/A converter, for example, by using either binary-weighted R, R-2R, or other configurations. Explain your selection criteria.

- Describe your design methods for the constant current source.

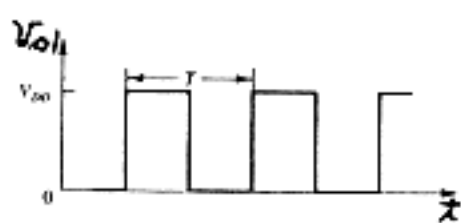


Fig. 3(a)

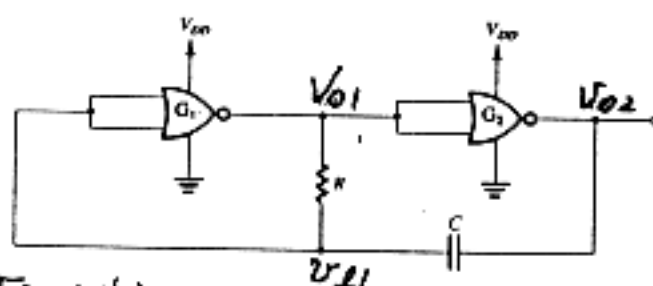


Fig. 3(b)