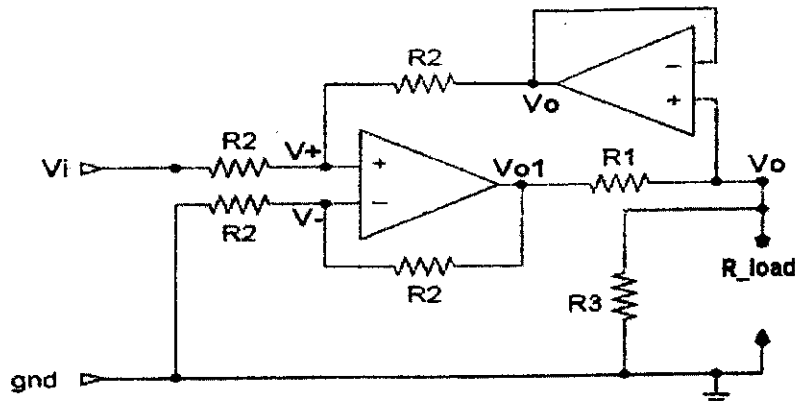



本試題是否可以使用計算機:  可使用,  不可使用 (請命題老師勾選)

1. (15 %) Explain the terminologies generally used in microelectronics:
- (a) Opto-isolator
  - (b) Register transfer logic (RTL) in IC design
  - (c) VHDL in IC design
  - (d) Electronic design automation (EDA)
  - (e) Switched-capacitor integrator



(Figure 1)

2. (15 %) Figure 1 is a modified Howland amplifier which has been designed to be a constant current pump (source) or a voltage to current converter.
- (a) Please show that the current across  $R_{load}$  is independent of  $R_{load}$  and  $R_3$ .
  - (b) Based on the modified Howland amplifier above, we wish to design a micro-processor controlled constant current mono-phase pulse of  $300 \mu s$  pulse width with 4096 steps current outputs at 1 kHz. Please draw your design in block diagram with necessary specifications. You can make any assumptions and use components that you are familiar with.
3. (20 %) Figure 2 shows a simple astable multivibrator using two ideal NOR CMOS gates.
- (a) Please draw the output of  $V_2$  with reference to  $V_3$  on the right hand side of Fig. 2.
  - (b) Derive the period ( $T$ ) of the astable multivibrator in terms of  $RC$ ,  $V_{DD}$  and  $V_{th}$ .
  - (c) Please give your design such that the frequency of the astable multivibrator will be 1 kHz.

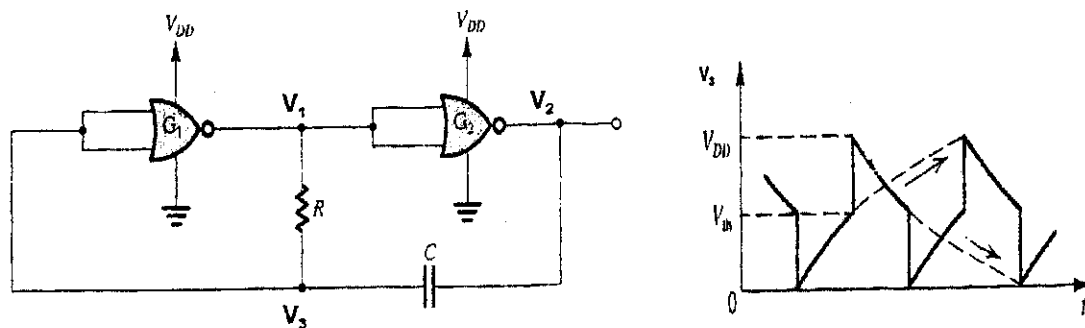


(Figure 2)

(背面仍有題目, 請繼續作答)

本試題是否可以使用計算機： 可使用， 不可使用 (請命題老師勾選)

4. (15 %) Sallen-Key filter is one of common filters with a single op-amp, as shown in Fig. 3.

- (a) Calculate the DC gain, K.
- (b) Derive the  $V_{out}/V_i$
- (c) Give your components that meet the requirement of a low pass filter at cut off frequency of 1 kHz.

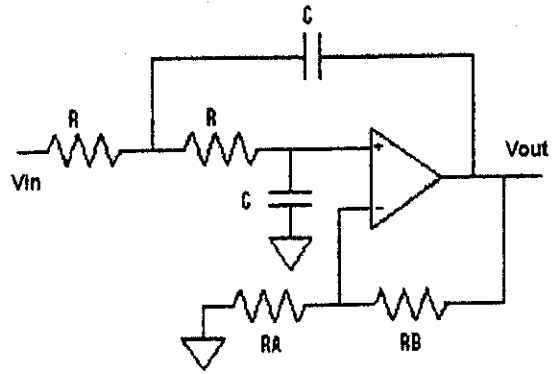

(Figure 3)


5. (15 %) In our laboratory, we wish to design a phase detector that can measure the phase difference between two sinusoidal waveforms at the same frequency.

- (a) First, please draw your design of a Wien bridge oscillator (or any other kind) that can generate sine wave source of 1 kHz.
- (b) Draw your design of the phase detector with the input and output signals. Describe your design considerations.

6. (20%) As shown in Fig. 4, a MOSFET can be biased by a constant-current source  $I_Q$ . The threshold voltage of the n-channel MOSFET is denoted as  $V_{TN}$ . The conduction parameter for the n-channel transistor is denoted as  $K_n$ .  $M_2$ ,  $M_3$ , and  $M_4$  with transistor parameters  $K_{n2}$ ,  $K_{n3}$ ,  $K_{n4}$ , form the current source.

$$\text{We can write } K_{n3} (V_{GS3} - V_{TN3})^2 = K_{n4} (V_{GS4} - V_{TN4})^2$$

- (a) Determine  $I_Q$  in terms of  $K_{n2}$ ,  $V_{GS3}$ ,  $V_{TN2}$
- (b) Assume that the threshold voltage of each transistor is  $V_{TN}=1$  V. Design the ratio of transistor parameters of  $M_4$  and  $M_3$ ,  $K_{n4}/K_{n3}$  such that  $V_{GS3} = 2$  V.
- (c) Determine the transistor parameter of  $M_2$ ,  $K_{n2}$  such that  $I_Q = 100 \mu\text{A}$ .

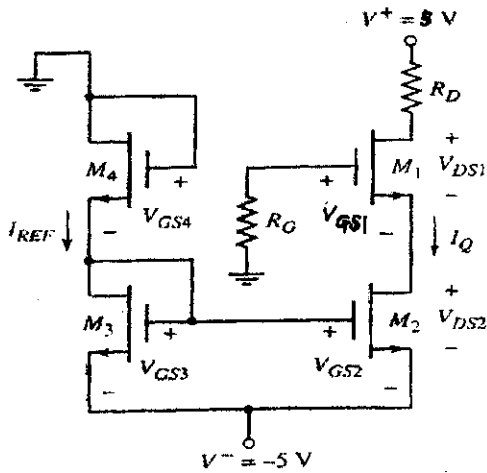

(Figure 4)