

1. A modified version of differential amplifier is shown in Fig. 1. The gain may be set by varying the resistor R_G . Please compute the differential voltage gain when $R_G = 5\text{ k}\Omega$, $R_1 = 100\text{ k}\Omega$, and $R_2 = 500\text{ k}\Omega$. (15%)
2. A feedback type of transconductance amplifier is depicted in Fig. 2. Find the input resistance of the one-port network. (10%)
3. Find I_p and I_n in a forward-biased diode with the forward conducting current $I = 1\text{ mA}$. The parameters for this diode are $N_A = 10^{18}/\text{cm}^3$, $N_D = 10^{16}/\text{cm}^3$, $L_p = 5\text{ }\mu\text{m}$, $L_n = 10\text{ }\mu\text{m}$, $D_p = 10\text{ cm}^2/\text{s}$, and $D_n = 20\text{ cm}^2/\text{s}$. (15%)
4. For a capacitively coupled common-emitter amplifier as depicted in Fig. 3, find the midband gain, and the value of R_L that reduces the midband gain to half. (10%)
The parameters for this transistor are given as follows. $V_{CC} = V_{EE} = 10\text{ V}$, $I = 1\text{ mA}$, $R_B = 100\text{ k}\Omega$, $R_C = 8\text{ k}\Omega$, $R_{sig} = 5\text{ k}\Omega$, $R_L = 5\text{ k}\Omega$, $\beta_0 = 100$, $V_A = 100\text{ V}$, $C_\mu = 1\text{ pF}$, $f_T = 800\text{ MHz}$, and $r_x = 50\text{ }\Omega$.

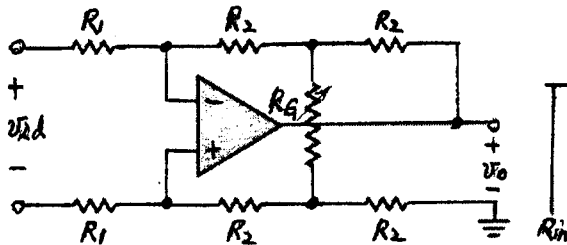


Fig. 1

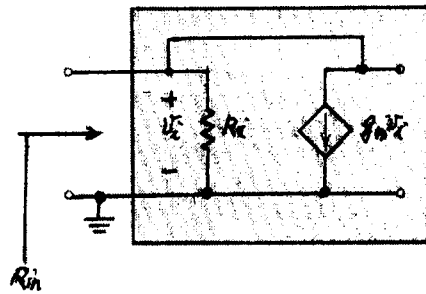


Fig. 2


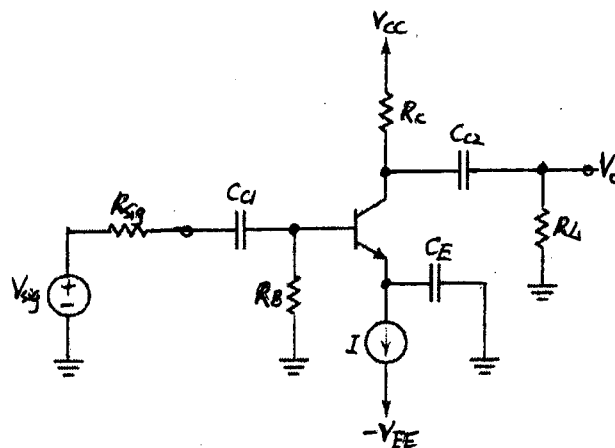


Fig. 3

(背面仍有題目,請繼續作答)

5. (15 %) Explain the following terminologies generally used in electronics

- (a) 1-line-to-8-line demultiplexer
- (b) Tristate buffer
- (c) Class E amplifier
- (d) Hardware description language (HDL)
- (e) Synchronous counter

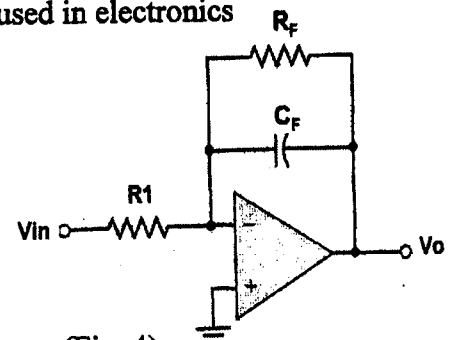


(Fig. 4)

6. (20 %) Figure 4 is the one-pole low-pass filter.

- (a) Please derive the cutoff frequency and $V_o(s)/V_{in}(s)$
- (b) Please choose the values of components that it can filter out frequency beyond 100 Hz with gain of -1.
- (c) Draw the equivalent switched-capacitor filter of the same specifications of (b) giving the clock frequency (f_c) with equivalent resistance $R_{eq} = 1/f_c C$

7. (15 %) Figure 5 is an example trace of ECG waveform, an analogue signal recorded from human heart. You may make any assumptions in your designed circuit.

- (a) Could you design a hybrid circuit, combination of analogue and digital circuits, to determine the R-R interval, the t marked in the figure, up to the time resolution of ms? (Hint: comparator and counter might be a good combination)
- (b) Could you design a circuit to provide the analogue output of the peak-to-peak amplitude, marked with x's? (Hint: peak detectors, summer, inverter of OP-Amps might be needed)

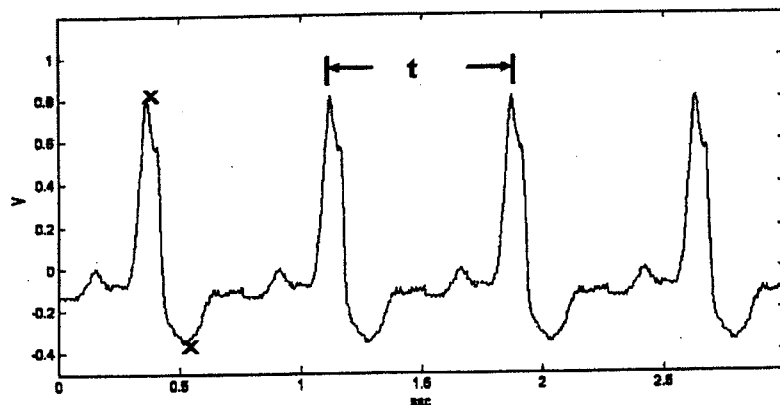

(Fig. 5)