

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. The circuit of Fig. 1 is used to create an ac-coupled noninverting amplifier with a gain of 100 V/V using resistor  $R_2$  of 100 k $\Omega$ .

(a) What values of  $R_1$  and  $R_3$  should be used ? (4%)

(b) For break frequency due to  $C_1$  at 100 Hz, and that due to  $C_2$  at 10 Hz, what values of  $C_1$  and  $C_2$  are needed ?(8%)

 


Fig. 1.

2. Consider an operational rectifier as shown in Fig. 2 with  $R=1$  k $\Omega$ . Assume that the op amp is ideal and that its output saturates at  $\pm 12$  V. The diode has a 0.7-V drop at 1-mA current. Find the voltages ( $V_A$  and  $V_O$ ) that result at the rectifier output ( $V_O$ ) and at the opamp output ( $V_A$ ) under the conditions:

(a)  $V_i=10$ mV (4%)

(b)  $V_i=1$ V (4%)

(c)  $V_i=-1$ V (4%)

 


Fig. 2

3. The CMOS cascade differential amplifier of Fig. 3 is fabricated in a  $0.18\text{-}\mu\text{m}$  technology for which  $\mu_n C_{ox} = 4\mu_p C_{ox} = 400 \mu\text{A}/\text{V}^2$ ,  $|V_t| = 0.5\text{V}$ , and  $|V_A'| = 10 \text{ V}/\mu\text{m}$ . Assume the bias current  $I = 100\mu\text{A}$ , and all transistors have a channel length twice the minimum length and are operating at  $|V_{ov}| = |V_{GS} - V_t| = 0.2\text{V}$ .
- Find  $W/L$  for each of  $Q_1$  to  $Q_4$  (4%)
  - Find  $W/L$  for each of  $Q_5$  to  $Q_8$  (4%)
  - Determine the differential voltage gain  $A_d (= v_{od}/v_{id})$  (4%)

 


Fig. 3

4. As shown in Fig. 4, all the MOS transistors in the feedback are sized to operate at  $|V_{ov}| = |V_{GS} - V_t| = 0.2 \text{ V}$ . For all transistors,  $|V_t| = 0.4\text{V}$  and early voltage  $= |V_A| = |1/\lambda| = 20\text{V}$ .
- Find the closed-loop gain of  $A_f (= I_o/V_S)$ . (4%)
  - Find the output impedance,  $R_{out}$ . (5%)
  - If the voltage at the source of  $Q_5$  is taken as the output ( $V_o$ ), find the voltage gain ( $V_o/V_S$ ) using the value of  $I_o/V_S$  obtained in (a). (5%)

 


Fig. 4

5. Explanatory questions:

- (a) Draw and explain the circuit diagram of a basic Wien-bridge oscillator. (5%)
- (b) A student mistakenly configures a Sallen and Key filter as shown in Fig. 5. Explain why this is not a useful circuit. (5%)

 


Fig. 5

6. Consider a three-pole feedback amplifier with a loop gain function given by

$$T(f) = \frac{1000}{(1 + j \frac{f}{10^4})(1 + j \frac{f}{10^6})(1 + j \frac{f}{10^8})}$$

- (a) Please draw the Bode plot of this amplifier. (5%)
  - (b) Insert an additional dominant pole (assuming all original poles do not change) such that the resulting phase margin is at least 45 degrees. (5%)
7. Consider the circuit shown in Fig. 6. Assume the saturated output voltages of op-amp are  $\pm 10V$ .
- (a) Find  $R_x$  such that the frequency of oscillation is 500 Hz when the potentiometer is connected to point A. (5%)
  - (b) Using the result of (a), determine the oscillator frequency when the potentiometer is connected to point B. (5%)

 


Fig. 6

8. For the op-amp circuit shown in Fig. 7, assume transistor parameters of  $|V_T|=0.5V$  (all transistors),  $K_n' (= \mu_n C_{ox}) = 100 \mu A/V^2$ ,  $K_p' (= \mu_p C_{ox}) = 40 \mu A/V^2$ , and circuit parameters of  $V^+ = 5V$ ,  $V^- = -5V$ ,  $R_{set} = 225 k\Omega$  and  $C_1 = 2pF$ . Given that the width-to-length ratios of transistor  $M_3/M_4 = 6.25$  and all other transistors have the same W/L ratios of 12.5.

- (a) Determine the dc bias currents of the input (i.e.  $M_1/M_2$ ) and second (i.e.  $M_7$ ) stages. (4%)
- (b) Assume  $\lambda (= 1/V_A) = 0.02V^{-1}$  for all transistors, find the small-signal voltage gains of the input and second stages, and the overall voltage gain of the op-amp. (5%)
- (c) Calculate the slew rate of this op-amp. (3%)

 


Fig. 7

9. Consider the switched-capacitor circuit shown in Fig. 8.

- (a) If the clock frequency is  $f_c = 100 kHz$  and  $C = 1.2 pF$ , what is the value of the simulated resistance? (4%)
- (b) A  $50M\Omega$  resistor is to be simulated using a clock frequency of  $f_c = 50 kHz$ . What is the required value of capacitor? (4%)

 


Fig. 8