

國立成功大學
111學年度碩士班招生考試試題

編 號： 180、192、197
電機工程學系
系 所： 電腦與通信工程研究所
電機資訊學院-微電、奈米聯招
科 目： 電子學
日 期： 0219
節 次： 第 1 節
備 註： 可使用計算機

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

- Fig. 1 shows an op amp connected in a closed loop with gain of +100 utilizing a feedback resistor of $1\text{M}\Omega$.
 - If the input bias current is 300 nA , what output voltage results with the input grounded? (4%)
 - If the input offset is $\pm 3\text{ mV}$ and the input bias current is 300 nA , what is the largest possible output voltage that can be observed with the input grounded? (4%)
 - If bias-current compensation is used, what is the value of the required resistor to be placed in series with the positive input lead? If the offset current is no more than one-tenth the bias current ($I_{OS}=30\text{ nA}$), what is the resulting output offset voltage due to offset current alone? (8%)
 - With bias-current compensation as in (c) in place, what is the largest dc voltage at the output due to the combined effect of offset voltage and offset current? (4%)

 


Fig. 1

- The two-stage CMOS op amp in Fig. 2 is fabricated in a $0.18\text{-}\mu\text{m}$ technology with $V_{tn} = -V_{tp} = 0.6\text{ V}$. If each of $Q_1, Q_2, Q_3,$ and Q_4 is conducting a drain current of $100\text{ }\mu\text{A}$ and each of Q_5 and Q_7 is conducting a current of $200\text{ }\mu\text{A}$. Assume that all transistors operate at 0.2-V overdrive voltages ($V_{ov}=V_{GS}-V_{tn}=0.2\text{ V}$).
 - Find the input common-mode voltage. (4%)
 - Find the allowable range of the output voltage. (4%)
 - With $v_A=v_{id}/2$ and $v_B=-v_{id}/2$, find the voltage gain v_o/v_{id} . Assume an Early voltage of 10 V . (4%)

 


Fig. 2

3. Fig. 3 shows a shunt-shunt feedback amplifier. The MOSFETs have threshold voltage $V_{th}=0.6$ V, Early voltage $V_A=20$ V, and $\mu_n C_{ox}=200 \mu\text{A}/\text{V}^2$. The power supply voltage $V_{DD}=3.3$ V, and $R_L=2$ k Ω . The coupling capacitor C_C can be assumed to be very large.

- Perform a dc design to meet the following specifications: $I_{D1}=100 \mu\text{A}$, $I_{D2}=1$ mA, $I_{R2,R1}=10 \mu\text{A}$, overdrive voltage $V_{ov1,2}=V_{GS1,2}-V_{th}=0.2$ V. Neglect the Early effect. Specify the values required for R_1 and R_2 (4%)
- Find the value of R_S that results in V_O/V_S being ideally -6 V/V (2%)
- Find the values of open-loop gain A , input resistance R_i , and output resistance R_o from open-loop circuit (6%)
- Find the value obtained for V_O/V_S (2%)
- Find R_{in} and R_{out} in Fig. 3 (4%)

 


Fig. 3

4. Consider the circuit of Fig. 4. Given the op amps have saturation voltages of ± 10 V and $C=0.01 \mu\text{F}$, $R_1=20$ k Ω , $R_2=10$ k Ω .

- Sketch and label the waveforms (peak amplitude required) of v_{o1} and v_o . (8%)
- Find the value of R_3 such that the resulted waveform frequency equals 1 kHz. (4%)

 


Fig. 4

5. The CMOS output stage of Fig. 5 is designed to operate at $I_Q=1\text{ mA}$ with $I_{BIAS}=0.1\text{ mA}$. Assume that Q_1 and Q_2 are matched and Q_N and Q_P are matched, and each transistor operates at an overdrive voltage of 0.15 V in the quiescent state. Let $\mu_n C_{ox}=250\text{ }\mu\text{A/V}^2$, $\mu_p C_{ox}=100\text{ }\mu\text{A/V}^2$, $V_{tn}=-V_{tp}=0.45\text{ V}$, and $V_{DD}=V_{SS}=2.5\text{ V}$.
- What kind of this output stage is (Hint: Class A, B, AB, C)? (3%)
 - Specify the (W/L) ratio for Q_1 , Q_2 , Q_N , and Q_P . (8%)
 - In the quiescent state with $v_O=0\text{ V}$, what must $v_{i\text{be}}$ be? (4%)
 - If this output stage is required to supply a maximum load of 10 mA to R_L , find the maximum allowable output voltage (assume that I_{BIAS} needs a minimum of 0.2 V to operate properly). (5%)

 


Fig. 5

6. For the filter circuit shown in Fig. 6, assuming the transconductance amplifiers are ideal.

- Derive the transfer function: $\frac{V_o(s)}{V_i(s)}$ (3%)
- Based on (a), find the values of G_{m1} and G_{m2} to achieve a low-pass filter with a pole frequency of 20 MHz and a DC gain of 10 . Given $C=2\text{ pF}$. (6%)

 


Fig. 6

編號：180、192、197

國立成功大學 111 學年度碩士班招生考試試題

系 所：電機工程學系、電腦與通信工程研究所、電機資訊學院、微電子、奈米科技

考試科目：電子學

考試日期：0219，節次：1

第 4 頁，共 4 頁

7. For the 2nd order filter circuit shown in Fig. 7, assuming the op amps are ideal. Given $C_1=C_2=10$ nF, $R_3=14.14$ k Ω , and $R_4=7.07$ k Ω . Please find out the following filter's characteristics:

- (a) High-frequency gain (3%)
- (b) ω_0 (pole frequency, unit: rad/sec) (3%)
- (c) Q (pole quality factor) (3%)

 


Fig. 7