

國立成功大學

114學年度碩士班招生考試試題

編 號： 133、142、145

系 所： 電機工程學系
電腦與通信工程研究所
電機資訊學院-微電、奈米聯招

科 目： 電子學

日 期： 0210

節 次： 第 1 節

注 意： 1. 可使用計算機
2. 請於答案卷(卡)作答，於
試題上作答，不予計分。

1. The common-source (CS) amplifier in Fig. 1 is biased to operate at $g_m=5$ mA/V, and has the following component values: $R_{sig}=100$ k Ω , $R_{G1}=47$ M Ω , $R_{G2}=10$ M Ω , $C_{C1}=0.01$ μ F, $R_S=2$ k Ω , $C_S=10$ μ F, $R_D=4.7$ k Ω , $R_L=10$ k Ω , and $C_{C2}=1$ μ F. Neglect r_o and find (a) gain ($A_M=V_o/V_{sig}$), (b) input pole (f_{p1}), (c) source pole (f_{p2}), (d) source zero (f_z), (e) output pole (f_{p3}), and (f) -3dB frequency (f_L). (30%)

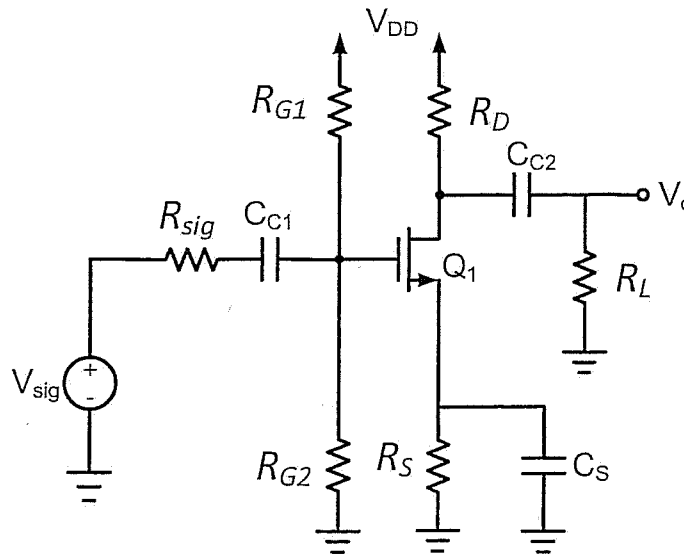


Fig. 1

2. The circuit in Fig. 2 utilizes a voltage amplifier with gain μ in a shunt-shunt feedback topology with a feedback network composed of resistor $R_F=20$ k Ω , input resistor $R_S=2$ k Ω , and load resistor $R_L=\infty$.
- (a) If the amplifier μ has a DC gain of 10^3 V/V, an input resistance $R_{id}=100$ k Ω , and an output resistance $r_o=2$ k Ω , find the actual V_o/V_S realized. Also, find R_{in} and R_{out} . (15%)
- (b) If the amplifier μ has an upper -3dB frequency of 1 KHz and a uniform -20-dB/decade gain rolloff, what is the 3-dB frequency of the gain $|V_o/V_S|$. (5%)

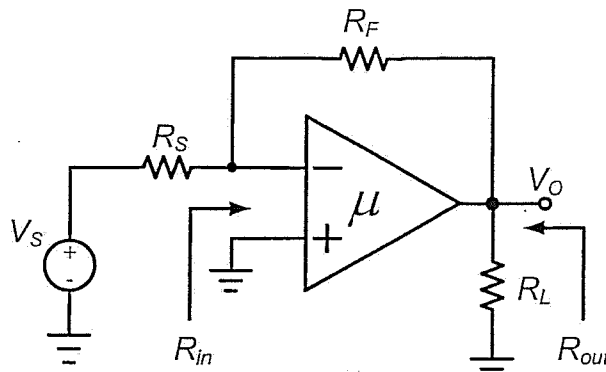


Fig. 2

3. Please design a two-stage CMOS op amp, as shown in Fig. 3, for obtaining a dc gain of 4000 V/V. Assume that the available fabrication technology is of the 0.5- μm type for which $V_{tn} = |V_{tp}| = 0.5\text{ V}$, $k_n' = 200\ \mu\text{A}/\text{V}^2$, $k_p' = 80\ \mu\text{A}/\text{V}^2$, $V_{An} = |V_{Ap}| = 20\ \text{V}/\mu\text{m}$, and $V_{DD} = |V_{SS}| = 1.65\text{ V}$. To achieve a reasonable dc gain per stage, use $L = 1\ \mu\text{m}$ for all devices. Also, for simplicity, operate all devices at the same $|V_{OV}|$, in the range of 0.2 V to 0.4 V. The current is given to be $I = 200\ \mu\text{A}$ and $I_{D6} = 500\ \mu\text{A}$, and C_C is 1.8 pF.

Please give the values realized for the following parameters (4% each)

- (a) input common-mode range,
- (b) maximum possible range of the output swing,
- (c) output resistance R_o ,
- (d) common-mode rejection ratio (CMRR),
- (e) power-supply rejection ratio PSRR+,
- (f) power-supply rejection ratio PSRR-,
- (g) slew rate (SR),
- (h) unit-gain frequency (ft).

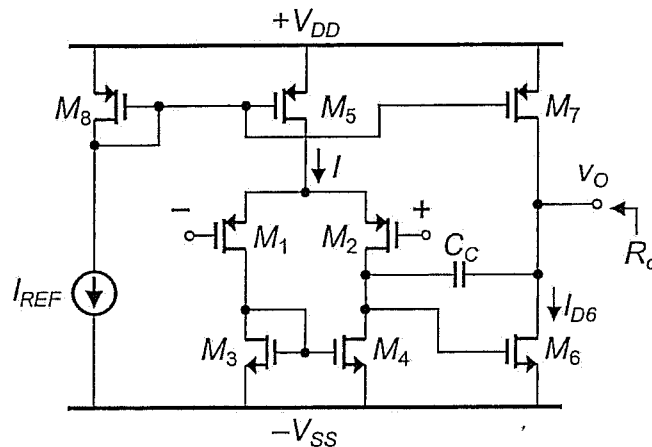


Fig. 3

4. For the quadrature oscillator shown in Fig. 4, please briefly answer the questions (a)-(f), (3% each)

- (a) What is the function of the circuit enclosed in the dash-circle line 1?
- (b) What is the function of the circuit enclosed in the dash-circle line 2?
- (c) What is the function of the circuit enclosed in the dash-circle line 3?
- (d) Which value of R_f should we use for maintaining the oscillation?
- (e) Follow 4(d), what is the oscillation frequency ω_0 ?
- (f) What is the phase difference of the sinusoidal signals of v_{O1} and v_{O2} ?

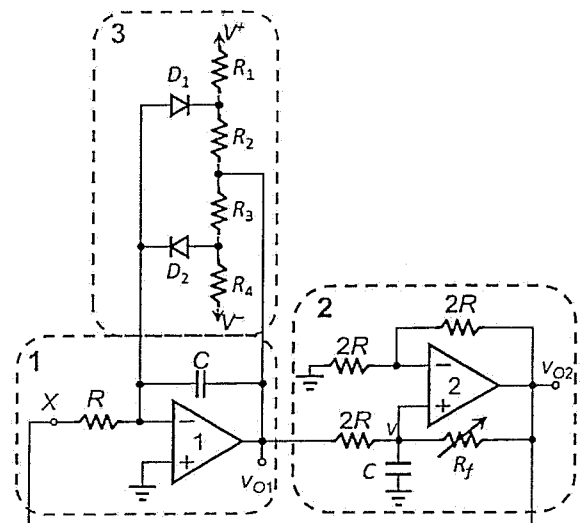


Fig. 4