

國立成功大學
110學年度碩士班招生考試試題

編 號： 192

系 所： 電腦與通信工程研究所

科 目： 電子學

日 期： 0203

節 次： 第 1 節

備 註： 可使用計算機

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. Derive the transfer function of the circuit in Fig. 1 with an ideal op amp and show that it can be written in the form $\frac{V_o}{V_i} = -\frac{R_2/R_1}{[1 + (\omega_1/j\omega)][1 + (j\omega/\omega_2)]}$

(a) Assume that the circuit is designed such that $\omega_2 \gg \omega_1$, what are the ω_1 and ω_2 ? (4%)

Find approximation expressions for the transfer function (V_o/V_i) in the following frequency regions:

(b) $\omega \ll \omega_1$ (4%)

(c) $\omega_1 \ll \omega \ll \omega_2$ (4%)

(d) $\omega \gg \omega_2$ (4%)

 


Fig. 1

2. A current-mirror-loaded MOS differential amplifier as shown in Fig. 2 is biased with a current source $I=0.2\text{mA}$. The two NMOS transistors of the differential pair are operating at overdrive voltage: $V_{ov}=V_{GS}-V_{tn}=0.2\text{V}$, and the PMOS device of the mirror are operating at overdrive voltage: $|V_{ov}|=|V_{GS}|-|V_{tp}|=0.2\text{V}$. The Early voltage $V_{An}=|V_{Ap}|=10\text{V}$. Assume $C_m=0.1\text{pF}$ and $C_L=0.2\text{pF}$.

(a) Find the dc gain of current-mirror-loaded MOS differential amplifier? (4%)

(b) Find the frequencies of the poles (f_{p1}, f_{p2}) and zero (f_z) of the current-mirror-loaded MOS differential amplifier? (12%)

 


Fig. 2

3. The transconductance amplifier in Fig. 3 utilizes a differential amplifier with gain μ and a very high input resistance. The differential amplifier drives a transistor Q characterized by its g_m and r_o . A resistor R_F senses the output current I_o . The open loop gain and closed loop gain are A and A_f , respectively, and the feedback factor is β .

- (a) For $A\beta \gg 1$, select a value for R_F that results in $A_f \equiv I_o/V_s \approx 5 \text{ mA/V}$. (2%)
- (b) Find the circuit and derive an expression for A. (4%)
- (c) Find A and A_f with $\mu=1000 \text{ V/V}$, $g_m=2 \text{ mA/V}$, $r_o=20 \text{ k}\Omega$, and the value of R_F you selected in (a). (4%)
- (d) Find values of R_o and R_{of} . (8%)

 


Fig. 3

4. For a dc voltage of 1V applied to the input of the switched-capacitor Filter shown in Fig. 4, in which C_1 is 1 pF, C_2 is 10 pF, and the frequency of the non-overlapping clocks (ϕ_1 and ϕ_2) is 100 kHz.
- (a) What charge is transferred for each cycle of the two-phase clock? (2%)
 - (b) What is the average current drawn from the input source? (2%)
 - (c) What change would you expect in the output for each cycle of the clock? (3%)
 - (d) What is the average slope of the staircase output voltage produced? (3%)

 


Fig. 4

5. [Butterworth Filter Approximation]

- (a) Find the Butterworth transfer function that meets the following low-pass filter specifications: passband edge frequency $f_p = 10$ kHz, stopband edge frequency $f_s = 40$ kHz, maximum allowed variation in passband transmission $A_{max} = 1$ dB, minimum required stopband attenuation $A_{min} = 28$ dB, and dc gain = 2. (15 %)
- (b) Follow (a), if A_{min} is to be exactly 28 dB, to what value can A_{max} be reduced. (5 %)

Some equations you may need during answering this question: $A(\omega_s) = 10 \log \left[1 + \epsilon^2 \left(\frac{\omega_s}{\omega_p} \right)^{2N} \right]$

$$\left[1 + \epsilon^2 \left(\frac{\omega_s}{\omega_p} \right)^{2N} \right]; \quad \epsilon = \sqrt{10^{A_{max}/10} - 1}; \quad \omega_0 = \omega_p (1/\epsilon)^{1/N}; \quad \text{and } T(s) = \frac{K \omega_0^N}{(s-p_1)(s-p_2)\dots(s-p_N)}$$

6. An op amp with an open-loop voltage gain of 80 dB and poles at 10^5 Hz, 10^6 Hz, and 2×10^6 Hz is to be compensated to be stable for unity β . Assume that the op amp incorporates an amplifier equivalent to that in Fig. 5, with $C_1 = 150$ pF, $C_2 = 5$ pF, and $g_m = 40$ mA/V, and that f_{p1} is caused by the input circuit and f_{p2} by the output circuit of this amplifier. Assume that R_1 and C_1 represent the total resistance and capacitance between node G and ground, and R_2 and C_2 represent the total resistance and capacitance between node D and ground, although they are not depicted here. If the target phase margin is 45° , please find the required value of the compensating Miller capacitance and the new frequency of the output pole. (20%)

 


Fig. 5