

本試題是否可以使用計算機： 可使用， 不可使用 (請命題老師勾選)

* Useful constants : $\epsilon_0 = 10^{-9}/36\pi$; $\mu_0 = 4\pi \times 10^{-7}$; $\eta_0 = 120\pi$

1. If a two-port network has the following S-parameters, determine the input SWR and the forward gain (or loss) in dB. (5%)

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \begin{bmatrix} 0.2 & 0.5 \\ 0.5 & 0.2 \end{bmatrix}$$



2. The illustration of the microstrip (transmission) line are shown in the following figures. The microstrip substrate and thickness are $\epsilon_r = 4$ and $h = 1\text{mm}$.

(a) Determine the line width (W) of the microstrip line to have $Z_0 = 50\Omega$

Use the simple parallel-plate formula with TEM wave approximation. (5%)

(b) To have a more accurate dimension of the microstrip length from the effective dielectric constant ϵ_{eff} derived from the quasi-TEM approximation. Determine the length L of a $\lambda/4$ microstrip line at $f = 1\text{GHz}$ if $\epsilon_{\text{eff}} = 3$. (5%)

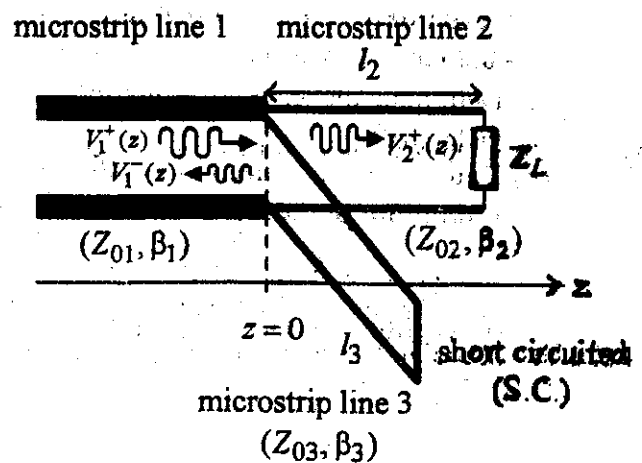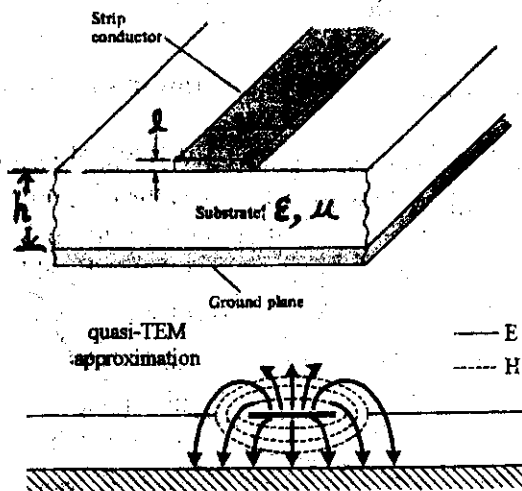(c) If $Z_{01} = 100\Omega$, $Z_{02} = Z_L = 50\Omega$ ($l_2 = 0.25\lambda$) and $Z_{03} = 200\Omega$ ($l_3 = 0.25\lambda$ with a short circuited load), If the voltage of the incident wave $V_1^+(z) = V_0 e^{-j\beta_1 z}$ is $V_0 = 1\text{V}$, determine the power P_L delivered to the load Z_L . (15%)




(背面仍有題目,請繼續作答)


本試題是否可以使用計算機: 可使用, 不可使用 (請命題老師勾選)

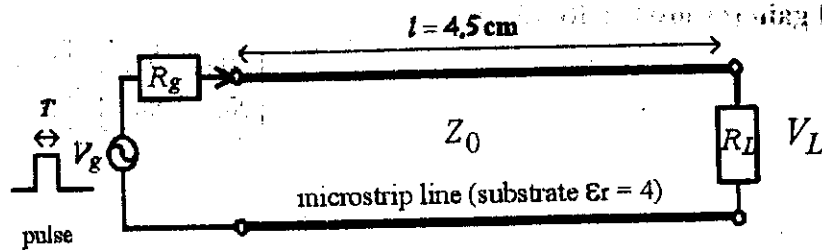3. As shown in the figure, a pulse signal is applied to a microstrip line (substrate $\epsilon_r = 4$) circuit. Plot the load voltage (V_L) waveform in the time domain (to $t = 1.2$ ns). (20%)

* Note: Use the simple parallel-plate TEM wave approximation to calculate the wave velocity (u_p) in the microstrip line.


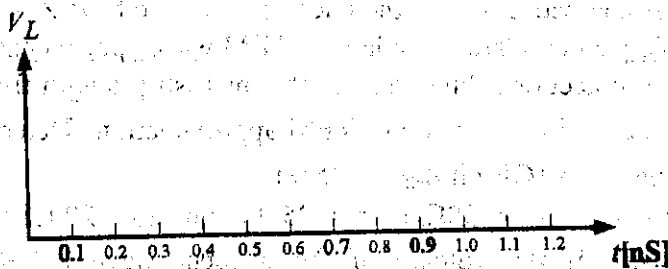
$$\begin{pmatrix} V_g = 9V \\ T = 0.1nS \end{pmatrix} \quad (R_g = 25\Omega, R_L = 100\Omega, Z_0 = 50\Omega)$$




4. A Ku-band (12-18 GHz) rectangular waveguide with the inner dimensions $a = 1.6$ cm and $b = 0.8$ cm is connected to a coaxial transmission line.
- Determine the length of a quarter-wavelength waveguide for the dominant mode at 15 GHz. (10%)
 - Determine the reflection coefficient Γ the coaxial-waveguide transition junction for the dominant mode at 15 GHz with a coaxial-line characteristic impedance $Z_0 = 50\Omega$. (10%)

Waveguide guided wavelength

$$\lambda_g = \lambda_0 / \sqrt{1 - (f_c/f)^2}$$

TE₁₀-mode guided impedance

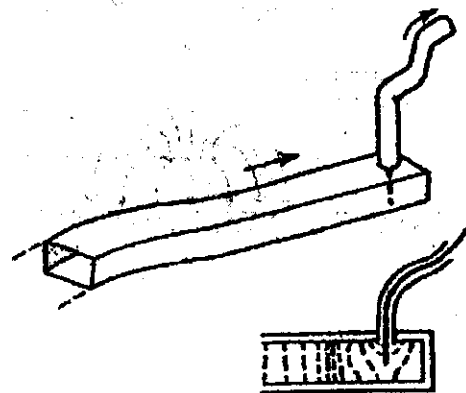
$$Z_{TE} = \eta_0 / \sqrt{1 - (f_c/f)^2}$$



Coaxial-to-waveguide transition

本試題是否可以使用計算機: 可使用, 不可使用 (請命題老師勾選)

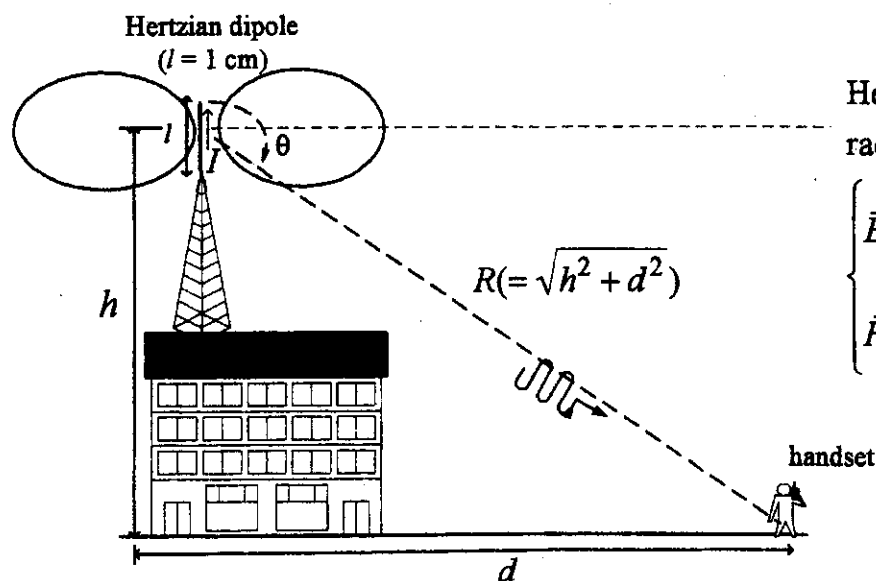5. As shown in the following figure, let the **input power** P_i to a base-station antenna (assuming to be a Hertzian dipole antenna with an uniform current distribution I) is $P_i = 10 \text{ W}$ and $f = 1 \text{ GHz}$, $h = 10 \text{ m}$.
- Determine the polarization of the far-zone radiated wave from this Hertzian dipole: vertical-, horizontal-, or circular-polarization? (5%)
 - If the input SWR of the antenna is $SWR = 3$ and the antenna radiation efficiency is $\eta_r = 0.8$, what is the radiation power P_{rad} of the antenna (with an input power $P_i = 10 \text{ W}$) (10%)
 - Determine the **radiation power density** p_{av} (or S) (W/m^2) from the Hertzian dipole antenna (with $I = 1 \text{ A}$) at a radio **handset** for a distance of $d = 1000 \text{ m}$. (10%)
 - From (c), if the allowed maximum radiation power density from the RF exposure safety standard for a human body is $S = 1 \text{ mW}/\text{cm}^2$, determine the safety distance d in the horizontal direction ($\theta = 90^\circ$) (5%)



Hertzian dipole far-zone radiation fields

$$\begin{cases} \vec{E} = \hat{\theta} j\eta_0 k I l \frac{e^{-jkR}}{4\pi R} \sin\theta \\ \vec{H} = \hat{\phi} jk I l \frac{e^{-jkR}}{4\pi R} \sin\theta \end{cases}$$