

1. (a) 4000 million electrons in 0.0002 second flow through one point in a line, calculate how much current is in a line. (10%), (b) 5000 million electrons takes $-0.02 \mu\text{J}$ to move from c point to d point, Find the voltage V_{cd} from c point to d point. $J=\text{Joule}$ (10%).
2. Use network transformation method to find R_{ab} and I in Figure 1. (20%)
3. In Figure 2, $V_s(t) = 5\cos(2.5 \cdot 10^8 t)$ V, (a) write down the differential equation by using $V_s(t)$, $V_1(t)$, and $V_o(t)$ (10%) and (b) solve the equation by Laplace transform and find $V_o(t)$ (15%). Assume zero initial conditions at capacitor.
4. Find three line currents in Figure 3 by using loop or mesh analysis. (20%).
5. Find the power delivering to the 40Ω resistor in Figure 4. (15%).

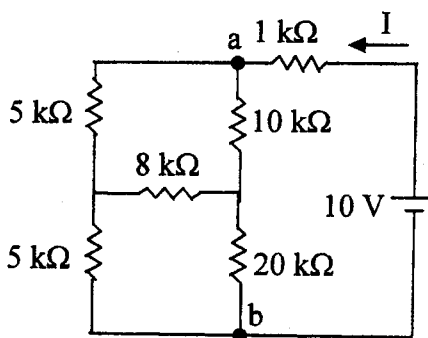


Figure 1

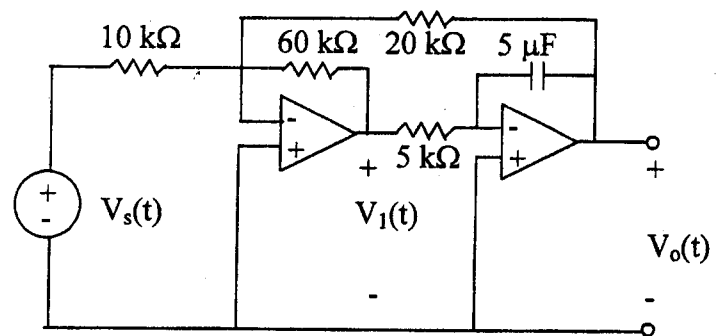


Figure 2

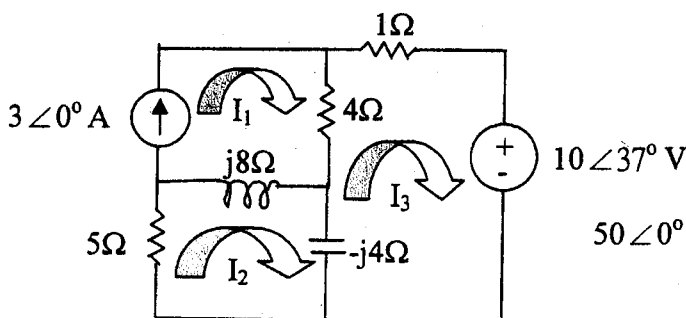


Figure 3

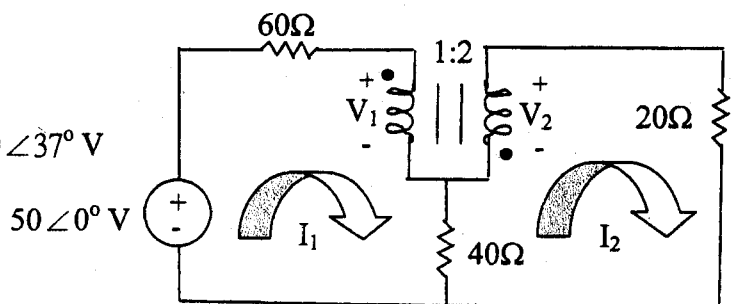


Figure 4