

甲、Describe KCL and KVL (Kirchhoff's Laws) (10%); in what conditions both laws sustain. (5%)

乙、Describe the superposition principle (5%); in what conditions the superposition principle sustain and prove it. (10%)

丙、In Figure A, $v_s(t) = u(t)$ (a unit step function), $i_1(0) = 1$, $i_2(0) = 0.6$, $v_c(0) = 0.5$, solve $i_2(t)$ by using the transformed circuit method (10%), write down the differential equation and solve $i_2(t)$ by using Laplace transform method. (10%) Both methods should conclude the same answer.

丁、Derive Y- Δ transformation formula by using node analysis. (20%).

戊、Describe Thevenin's and Norton's Theorems. (10%).

己、In Figure B, $v_s(t) = \cos(2t)u(t)$ ($u(t)$ is a unit step function), $i_1(0) = i_2(0) = 0$, find $i_1(t)$ and $i_2(t)$. (20%)

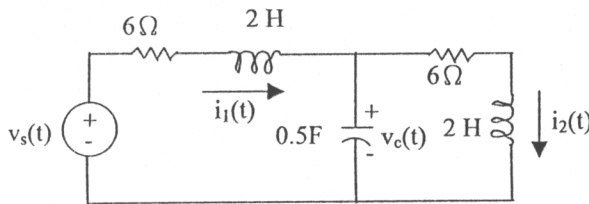


Figure A

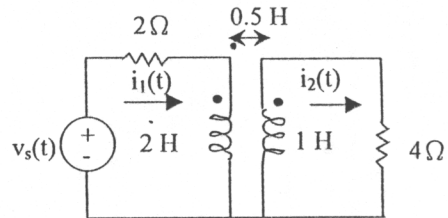


Figure B