

※ 考生請注意：本試題可使用計算機

1. Consider the circuit shown in Figure 1 with parameters of  $R_s=10\text{ k}\Omega$ ,  $R_i=10\text{ k}\Omega$ ,  $C_i=10\text{ pF}$ ,  $R_f=10\text{ k}\Omega$ ,  $R_2=20\text{ k}\Omega$ ,  $C_f=100\text{ nF}$  and  $G_m=100\text{ mA/V}$ .
  - (a) Find  $T_i(s) = V_i(s)/V_s(s)$  in the standard form of two polynomial expressions and the corresponding 3dB frequency. (6%)
  - (b) Find  $T(s) = V_o(s)/V_s(s)$  in the standard form of two polynomial expressions and the gain-bandwidth product. (10%)

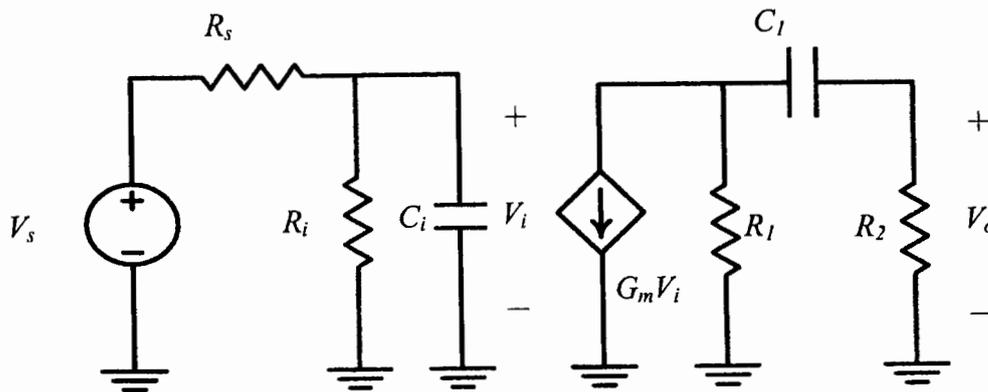


Figure 1

2. Consider the circuit shown in Figure 2 with parameters of  $V_{DD}=5\text{ V}$ ,  $\mu_n C_{ox}=40\text{ }\mu\text{ A/V}^2$ , and  $\mu_p C_{ox}=20\text{ }\mu\text{ A/V}^2$ ,  $|V_{tn0}|=|V_{tp0}|=1\text{ V}$ ,  $\gamma=0.5\text{ V}^{1/2}$ ,  $2\Phi_f=0.6\text{ V}$ ,  $(W/L)_{Q1}=2\text{ }\mu\text{ m}/1\text{ }\mu\text{ m}$ ,  $(W/L)_{Qp}=2 \times (W/L)_{Qn}=5\text{ }\mu\text{ m}/1\text{ }\mu\text{ m}$ ,  $C=10\text{ fF}$ .
  - (a) Determine threshold voltage of  $Q_1$  after  $v_i=V_{DD}$ ,  $v_C=V_{DD}$  and  $v_x$  is stable. (4%)
  - (b) Find noise margin  $V_{OH}$  of  $Q_1$  when  $v_i=V_{DD}$  and  $v_C=V_{DD}$ . (4%)
  - (c) Determine the static current of the inverter, its power consumption and  $v_o$  when  $v_i=V_{DD}$  and  $v_C=V_{DD}$ . (10%)

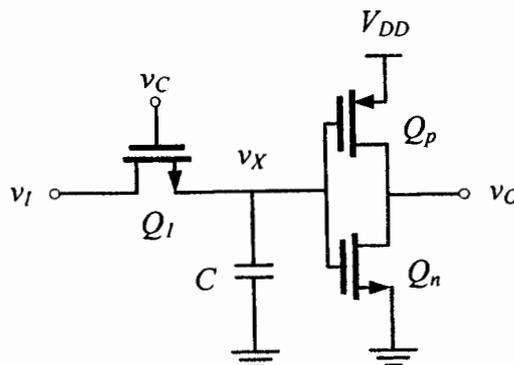


Figure 2

(背面仍有題目,請繼續作答)

※ 考生請注意：本試題可使用計算機

3. It is required to design the circuit of Figure 3 to provide a constant current  $I_O = 10\mu\text{A}$ .
- (a) Determine the values of the required resistors  $R_2$  and  $R_3$ , assuming that  $I_{REF} = 100\mu\text{A}$ ,  $V_{BE} = 0.7\text{V}$  at a 1-mA current, and  $\beta$  to be high. (6%)
- (b) If  $\beta = 200$  and  $V_A = 100\text{V}$ , find the value of the output resistance, and find the change in output current corresponding to a 5-V change in output voltage. (6%)

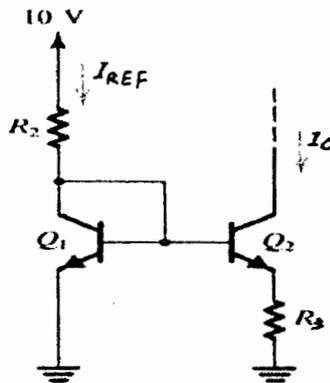


Figure 3

4. It is required to design the circuit of Figure 4 to provide a bias current  $I_B = 225\mu\text{A}$  with  $Q_8$  and  $Q_9$  as matched devices having  $W/L = 60/0.5$ . Transistors  $Q_{10}$ ,  $Q_{11}$ , and  $Q_{13}$  are to be identical, with the same  $g_m$  as  $Q_8$  and  $Q_9$ . Transistor  $Q_{12}$  is to be four times as wide as  $Q_{13}$ . Let  $\mu_n C_{ox} = 3\mu\text{p}C_{ox} = 180\mu\text{A}/\text{V}^2$  and  $V_{DD} = V_{SS} = 1.5\text{V}$ .
- (a) Find the required value of  $R_B$  and the voltage drop across  $R_B$ . (4%)
- (b) Specify the  $W/L$  ratios of  $Q_{10}$ ,  $Q_{11}$ ,  $Q_{12}$ , and  $Q_{13}$ . (3%)
- (c) Give the expected dc voltages at the gates of  $Q_{12}$ ,  $Q_{10}$ , and  $Q_8$ . (6%)

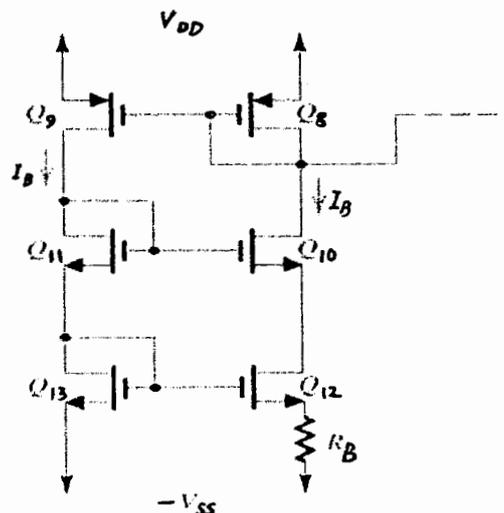


Figure 4

※ 考生請注意：本試題可使用計算機

5. Consider a feedback amplifier for which the open-loop gain  $A(s)$  is given by

$$A(s) = \frac{1000}{(1 + s/10^4)(1 + s/10^5)^2}$$

If the feedback factor  $\beta$  is independent of frequency, find the frequency at which the phase shift is  $180^\circ$ , and find the critical value of  $\beta$  at which oscillation will occur. (8%)

6. An amplifier has a dc gain of  $10^5$  and poles at  $5 \times 10^5$  Hz,  $10^7$  Hz, and  $5 \times 10^8$  Hz. To stabilize the amplifier with unity feedback ( $\beta = 1$ ), move the first pole by introducing a compensation capacitor. Assume the second pole remains. Calculate the frequency of the first new pole to achieve a phase margin of  $45^\circ$ . (5%)

7. A prototype active filter with admittances  $Y_1$  through  $Y_4$  is shown in Figure 7a. Assume the Opamp is ideal. The transfer function of this filter is as follows

$$\frac{v_o(s)}{v_i(s)} = \frac{Y_1 Y_2}{Y_1 Y_2 + Y_4 (Y_1 + Y_2 + Y_3)}$$

A designed filter is the cascade of the prototype circuits shown in Figure 7b, where  $R = 10 \text{ k}\Omega$ ,  $C = 0.01 \mu\text{F}$ ,  $C_1 = 1.082C$ ,  $C_2 = 0.9241C$ ,  $C_3 = 2.613C$ ,  $C_4 = 0.3825C$

- (a) Calculate the zeros and poles of the transfer function for this designed filter. (8%)  
 (b) What is the type of this filter (lowpass, highpass, bandpass, bandreject, or ...)? Explain why? (5%)

※ 考生請注意：本試題可使用計算機

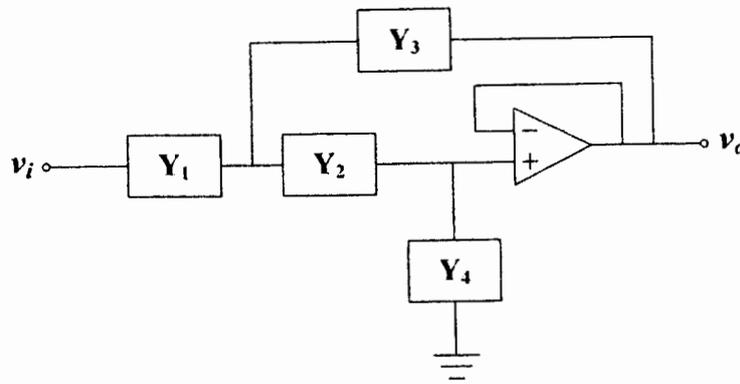


Figure 7a

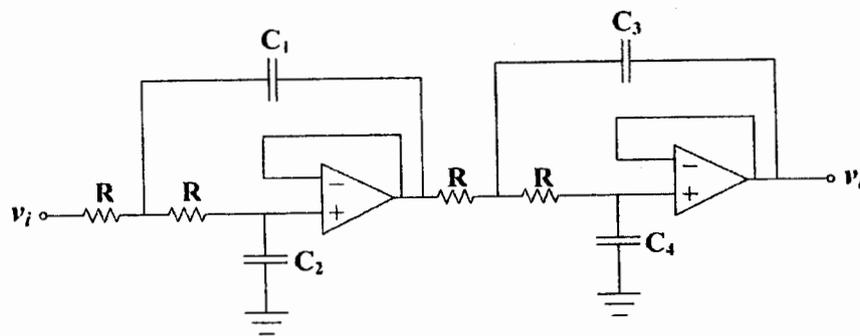


Figure 7b

8. A phase-shift oscillator is shown in Figure 8, where  $R = 10 \text{ k}\Omega$ ,  $C = 10 \text{ nF}$
- Find the loop gain by breaking the circuit at node X. (10%)
  - Calculate the oscillation frequency  $f_o$ , and the minimum required value of  $R_f$  for oscillation to start in this circuit. (5%)

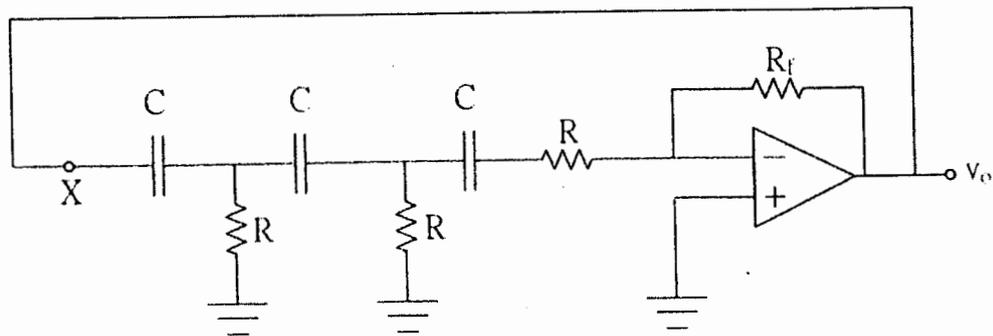


Figure 8