

- Determine the logic function at the output Y of the circuit shown in Fig. 1A. (10%)
 - What is the logic function realized at Y in the NMOS circuit shown in Fig. 1B? (10%)
- Using the ideal op amp to implement two different non-inverting integrators without inverter. Explain your results in brief. (10%)
- The op amp in the circuit of Fig. 2 has an open-loop gain of 10^5 and a single-pole rolloff with $\omega_{3dB} = 10$ rad/s.

 - Sketch a Bode plot for the loop gain. (2%)
 - Find the frequency at which $|A\beta| = 1$, and find the corresponding phase margin. (4%)
 - Find the closed-loop transfer function, including its zero and poles. (4%)
- Why is Miller-effect compensation often employed to compensate an op amp? (10%)

 


Fig. 1A

 


Fig. 1B

 


Fig. 2

(背面仍有題目,請繼續作答)

5. Draw the circuit diagram of a 2-bit charge-redistribution A/D converter and explain its operational principle. (10%)
6. The circuit of an amplifier is shown in Fig. 3.
 - (a) Express the overall small-signal gain v_o/v_i as a function of R_S , R_C , β , V_A , and collector current I_C . (10%)
 - (b) Assume that $R_S = R_C = 50\text{K}\Omega$, $\beta = 200$, $V_A = 120\text{V}$, determine the value of dc collector bias current I_C that maximizes v_o/v_i . (10%)
7. Calculate the bias current I_{bias} of the circuit shown in Fig. 4. Assume that threshold voltage of M1 and M2 is identical, $\mu_n C_{\text{ox}} = 20\mu\text{A}/\text{V}^2$. (10%)
8. Calculate the value of sensitivity S of output current to supply voltage for the circuit of Fig. 5, where $S = (V_{CC}/I_o)(\partial I_o/\partial V_{CC})$. Assume $V_{\text{BE(on)}} = 0.7\text{V}$. (10%)

 


Fig. 3

 


Fig. 4

 


Fig. 5