

1. (a) For the source follower in Fig.1 (a), find the open-circuit voltage gain v_{o1}/v_i and the output resistance R_{o1} , in terms of g_{m1} and χ . Neglect the effect of r_{o1} and that of the output resistance of the bias current source. $g_{mb} = \chi g_m$, g_{mb} is the body transconductance.
 - (b) For the common-gate amplifier in Fig.1(b), find the voltage gain v_o/v_{i2} and the input resistance R_i , in terms of g_{m2} , χ , and R . Neglect the effect of r_{o2} and that of the output resistance of the bias current source.
 - (c) If the output terminal of the source follower in (a) is connected to the input terminal of common-gate amplifier in (b), find the overall voltage gain v_o/v_i of the cascaded amplifier.
 - (d) If $V_{DD} = 5$ V and the dc bias voltage at the drain of Q_2 is to be 0 V, find the effective voltage ($V_{GS} - V_t$) required for Q_1 and Q_2 so that an overall voltage gain of 25 V/V is realized.
 - (e) For $I = 50 \mu A$ and $k_n = \mu_n C_{ox} = 50 \mu A/V^2$, find R and the (W/L) required for Q_1 and Q_2 . (15%)
2. As the circuit shown in Fig. 2, design the circuit to obtain a dc gain of 40 dB, a 3-dB frequency of 1.5 KHz., and an input resistance of 1 K Ω . At what frequency does the magnitude of transmission become unity? What is the phase angle at this frequency? Assume op amp is ideal. (10%)

 


Fig. 1

 


Fig. 2

3. (a) List five characteristics of an amplifier that are modified by negative feedback. (10%)
 - (b) Draw the circuit diagram of a switched-capacitor (SC) integrator. (5%)
 - (c) Derive the time constant of a SC integrator. (5%)
 - (d) Briefly explain why the time constant of a SC circuit can be well controlled. (5%)
4. If the collector current of a BJT operated in forward active region is expressed as $i_C = (a v_{BE}^2 + b v_{BE})(1 + c v_{CE}) \approx \beta i_B$, where a , b , c , and β are constant, derive and sketch its small-signal equivalent circuit for the cases of (a) $c = 0$ and (b) $c \neq 0$. (10%)

(背面仍有題目,請繼續作答)

5. (a) Design a MOSFET current mirror to provide currents of I_o and $I_o/2$ simultaneously, where I_o is a constant. (5%)
- (b) Derive the transfer characteristics (i.e., $v_o - v_i$ relation) of the circuit shown in Fig. 3. Assume the Op-Amp is ideal. (5%)
- (c) Draw the load line of the diode D_2 shown in Fig. 4 and find I graphically. Assume D_1 and D_2 are identical diodes, $V_A = 1.5V_y$, where V_y is the cut-in voltage of the diode. (5%)

 


Fig. 3



 


Fig. 4

 
6. An inverter circuit is shown in Fig. a. The output current-voltage characteristics of transistors Q1 and Q2, and the transfer characteristics of this inverter are shown in Fig. b, c, and d, respectively. Assume that $C_{tot} = 0.3\text{pF}$ and the input signal has $V(0) = 0.3\text{V}$ and $V(1) = 6\text{V}$. Please determine the values of the propagation delay t_{PHL} and t_{PLH} . (25%)




(a)

 

(b)

 

(c)

 

(d)