

1. (a) Draw the load line of D1 and find V_1 for the circuit shown in Fig. 1. Assume that D1, D2 and D3 have the same I-V characteristics, and $V_A = 3V_r$, where V_r is the cut-in voltage of the diode. (10%)
 (b) Derive and plot the small-signal equivalent circuit for a BJT with I-V characteristics expressed as $i_C = av_{BE}^2(1 + bv_{CE})$, where a and b are constant. (5%)
 (c) Determine I_D and V_O for the circuit shown in Fig. 2 for $V_{DD} = 5V$ and $V_1 = 2V$. Assume that $k_{n1} = 5k_{n2} = 50 \mu A/V^2$ and $V_{th1} = V_{th2} = 1V$, where $k_n (= 0.5 \mu_n C_{ox} (W/L))$ is the conduction parameter and V_{th} is the threshold voltage. Note that T2 is an enhancement-mode MOSFET. (10%)

 


Fig.1

 


Fig.2

2. Consider an OPAMP with $V_{DD}=5V$, $GND=0V$ and $V_{ss} = -5V$ as shown in Fig.3.
 (a) If $R_1=R_2=1k\Omega$ and $V_{in}=0V$, please find that $V_o=?$ when the OPAMP is with 10 mV input offset and gain $A=\infty$. (10%)(V_i is the inverting input node of the OPAMP)
 (b) If $R_1=R_2=1k\Omega$ and $V_{in}=2V$, please find that $V_o=?$ when the OPAMP is with 10 mV input offset and gain $A=\infty$. (5%)
 (c) If $R_1=1k\Omega$ and $R_2=1000k\Omega$, please find that $A_F=V_o/V_{in}=?$ when the OPAMP is with no offset and gain $A=100$.(10%)
3. For the circuit shown in Fig.4, for the BJT, $\beta=200$ and $|V_A| = 100V$, and for the MOSFET, $|V_A| = 30V$, $|V_t| = 1V$, $k'(W/L) = 200 \mu A/V^2$. Let $I=20\mu A$ and $V_{BIAS}=2V$. Assume the current generator I to have the same resistance as the output resistance of its connected circuit and assume the current generator $2I$ to be ideal. Find
 (a) the bias current in Q1 (3%);
 (b) the voltage at the node between the two transistors (assume $|V_{BE}| = 0.7V$) (3%);
 (c) g_m and r_o for each device (4%);
 (d) the maximum allowed value of v_o (3%);
 (e) the voltage gain (3%);
 (f) the input resistance(3%);
 (g) the output resistance (3%);
 (h) Does the current source $2I$ have to be a sophisticated one? For this generator, what output resistance would reduce the overall gain by 1%?(3%)

(背面仍有題目,請繼續作答)

4. A TTL NAND gate with a totem-pole output is shown in Fig.5. Assume that the inputs are derived from the outputs of identical gates and $\beta_F=100$ and $\beta_R=0.5$.
- (a) Given $A=B=C=V(1)$, determine the operation modes of transistors Q_1 and Q_4 . (4%)
 - (b) Repeat (a) for the situation where at least one input logic level is $V(0)$. (4%)
 - (c) Determine the logic levels. (8%)
 - (d) Please estimate the average static power dissipation (P_{av}) and dynamic power dissipation (P_{dyn}) per gate. (9%)

