

本試題是否可以使用計算機:  可使用,  不可使用 (請命題老師勾選)

- The characteristics for transistors  $Q_1$  and  $Q_2$ , used in the circuit shown in Fig. 1, are given in Figs. 2 and 3, respectively. Determine  $V_{DS1}$  and  $V_{DS2}$ . (13%)
- A TTL NAND gate with a totem-pole output is shown in Fig. 4. If all transistors are identical and the related parameters of transistor and diode are:  
 $V_{BE(cut-in)}=0.5V$ ,  $V_{BE(on)}=0.7V$ ,  $V_{BE(sat)}=0.8V$ ,  $V_{CE(sat)}=0.2V$ ,  $V_{DO(cut-in)}=0.6V$ ,  
 $V_{DO(on)}=0.7V$ . Please determine the average static power dissipation  $P_{(av)}$  and dynamic power dissipation  $P_{(dyn)}$  of this gate. (20%)

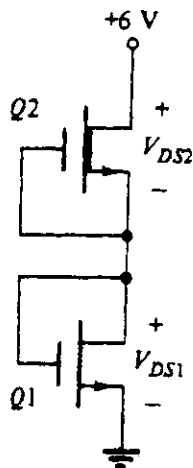


Fig. 1

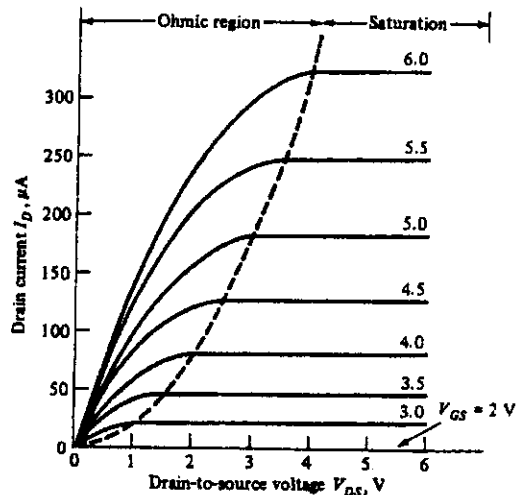


Fig. 2

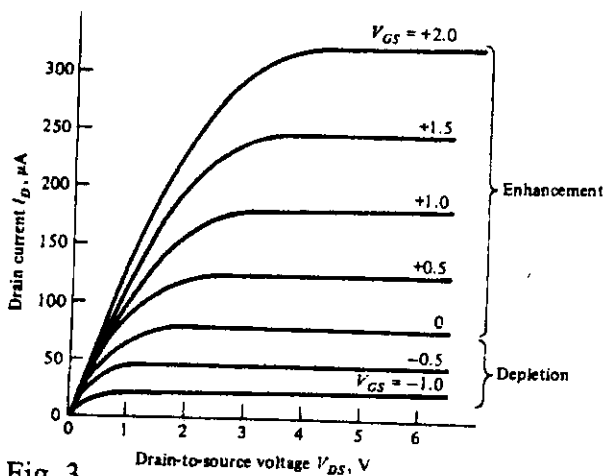


Fig. 3

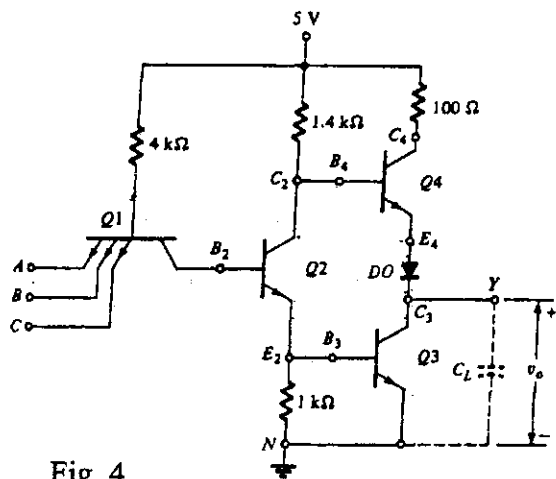


Fig. 4

- Please answer briefly for the following questions.
  - For class A, B, and AB amplifiers, which one has the maximum possible power conversion efficiency? Explain the condition that the maximum efficiency can be

(背面仍有題目, 請繼續作答)

本試題是否可以使用計算機:  可使用,  不可使用 (請命題老師勾選)

obtained in the amplifier. (3%)

- (b) List the four basic feedback topologies for amplifiers, which topology is desirable for the design of a current amplifier. (3%)
- (c) What is the function of CC in the CMOS op-amp circuit as shown in the attached Fig. 5? (3%)

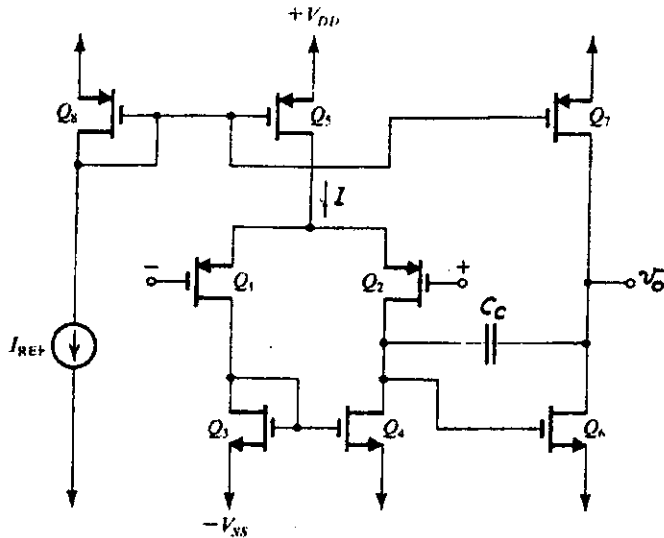


Fig. 5

4. Use the feedback method to analyze the circuit shown in the Fig. 6, Find
- (a) what is the feedback configuration of this circuit? (3%)
- (b) the feedback factor  $\beta$  and the voltage gain  $v_o/v_s$  (6%)
- (c) the input resistance  $R_{in}$  and the output resistance  $R_{out}$ . (6%)

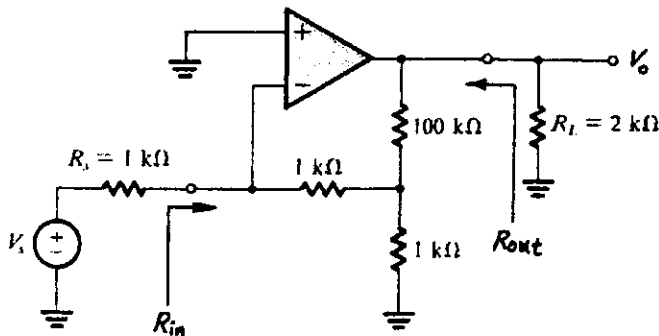


Fig. 6

The op-amp has open-loop gain  $\mu = 104$  v/v,  $R_{id} = 100$  k $\Omega$ ,  $r_o = 1$  k $\Omega$ .

5. For the circuit shown in Fig. 7, assume the diode voltage drop is 0.7V.
- (a) Show the analysis of this circuit that the oscillation can be obtained. (5%)
- (b) Find the frequency of oscillation, and the amplitude of the output sine wave in peak-to-peak value. (5%)

本試題是否可以使用計算機:  可使用,  不可使用 (請命題老師勾選)

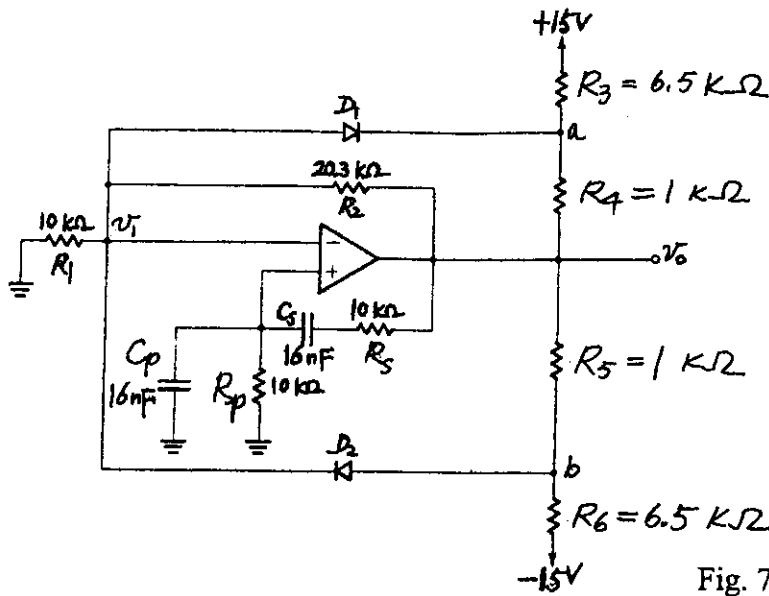


Fig. 7

6. Please answer or explain briefly the following questions.
- The reason why transistors could act as transfer resistances. (5%)
  - The bias condition for a transistor to operate as a linear amplifier. (5%)
  - For a CMOS inverter with matched MOSFETs having threshold voltage  $V_T=1$  V, find the noise margin if  $V_{DD}=5$  V. (5%)
  - What is the small-signal resistance of a diode biased to operate at a dc current  $I_D$ . (Assume the diode follows  $i_D = I_o (\exp(\frac{V_D}{V_T}) - 1)$ .) (5%)
7. (a) Draw the load line of  $D_2$  for the circuit shown in Fig. 8. Assume that  $D_1$  and  $D_2$  are matched diodes and  $V_A=4V_T$ , where  $V_T$  is the cut-in voltage of the diode. (10%)
- (b) State one of the possible methods to double the current  $I$ ? (3%)

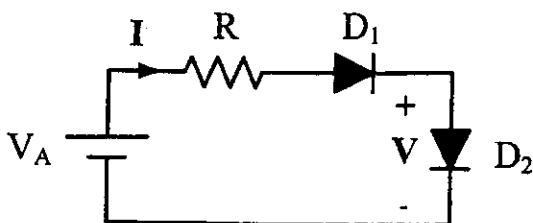


Fig. 8