

※ 考生請注意：本試題 可 不可 使用計算機

1. A full-wave rectifier circuit shown in Fig. 1 is to deliver 0.1 A and 15 V (average) to a load R. The ripple voltage is to be no larger than 0.4 V peak-to-peak. The input signal  $V_1$  is 120 V (rms) at 60 Hz. Assume diode turn-on voltages of 0.7 V. Determine the required turns ratio ( $N_1/N_2$ ) and the filter capacitance C value. (11%)
2. A CMOS inverter circuit shown in Fig. 2 has the parameters of  $V_{DD}=5$  V,  $V_{TN}=-V_{TP}=1$  V,  $K_N=100 \mu\text{A}/\text{V}^2$ , and  $K_P=50 \mu\text{A}/\text{V}^2$ . Determine the values of noise margins ( $NM_L, NM_H$ ) and the gate threshold voltage  $V_M$ . (22%)
3. (a) Explain briefly why BJTs and FETs can amplify ac signals? (6%)  
(b) Redefine the small-signal parameters of the transistor to absorb the emitter resistance  $R_E$  in Fig. 3 (i.e., to find  $g_{m2}, r_{\pi 2}$ , and  $r_{o2}$  in terms of  $g_{m1}, r_{\pi 1}$ , and  $r_{o1}$ ). (6%)  
(c) A single BJT amplifier is needed that has a gain of  $\sim 0$  dB and an input resistance of 25 M $\Omega$  with a load resistance of 25 k $\Omega$ . What is the preferred choice of amplifier configuration? Explain why you made this selection. (4%)
4. (a) Derive  $i_{out}$  and  $R_{out}$  for the circuit shown in Fig. 4. Assume the small-signal parameters of the MOSFET are  $g_m$  and  $r_o$ . (8%)  
(b) The MOSFETs in the circuit of Fig. 5 are matched, having  $k'_n(W/L)_1 = k'_p(W/L)_2 = 1.5 \text{ mA}/\text{V}^2$  and  $|V_t| = 0.5$  V. For G and D open, find the drain currents  $I_{D1}$  and  $I_{D2}$ . For  $r_o = \infty$ , what is the voltage gain of the amplifier from G to D? (10%)

(背面仍有題目,請繼續作答)

※ 考生請注意：本試題 可 不可 使用計算機

5. Consider the circuit as shown in Fig. 6. The circuit is biased with  $V_{cc} = 12\text{ V}$ , and the load resistance is  $R_L = 75\ \Omega$ .

The device parameters are :

$$I_{SD} = 5 \times 10^{-13}\text{ A for } D_1 \text{ and } D_2,$$

$$I_{SQ} = 2 \times 10^{-13}\text{ A, } \beta_n = \beta_p = 60 \text{ for } Q_n \text{ and } Q_p.$$

- (a) Neglecting base currents, determine the required value of  $I_{Bias}$  such that the quiescent currents in  $Q_n$  and  $Q_p$  are  $I_{CQ} = 5\text{ mA}$ . (6%)
- (b) Find  $i_{cn}$ ,  $i_{cp}$ ,  $V_{BE_n}$ ,  $V_{BE_p}$ , and  $I_D$  when  $V_o = 2\text{ V}$ . (8%)
- (c) What is the power conversion efficiency for this circuit when the output is a sinusoid and the peak output voltage reaches 80 percent of  $V_{cc}$ ? (8%)
6. Consider the phase-shift oscillator shown in Fig. 7, with parameters  $C = 100\text{ pF}$  and  $R = 10\text{ K}\Omega$ .
- (a) Determine the frequency of oscillation. (6%)
- (b) Find the minimum required value of  $R_2$  for sustaining oscillation. (5%)

※ 考生請注意：本試題 可 不可 使用計算機

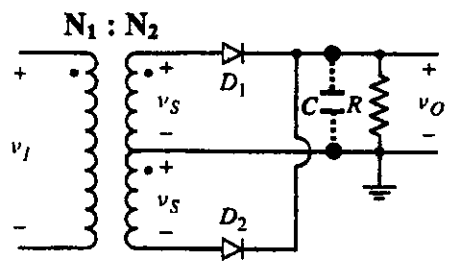


Fig. 1

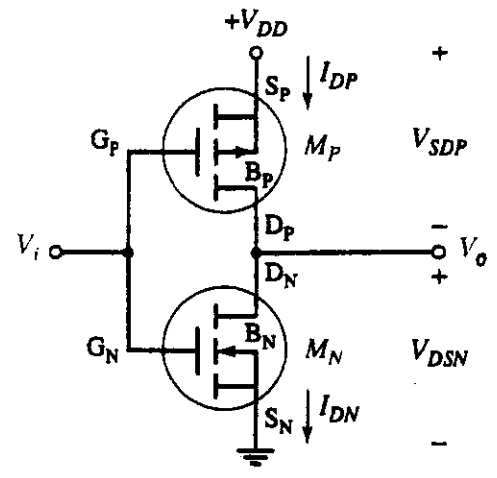


Fig. 2

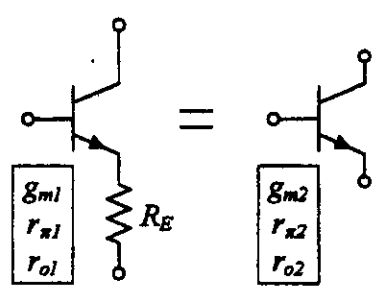


Fig. 3

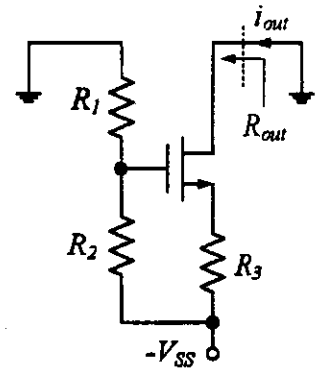


Fig. 4

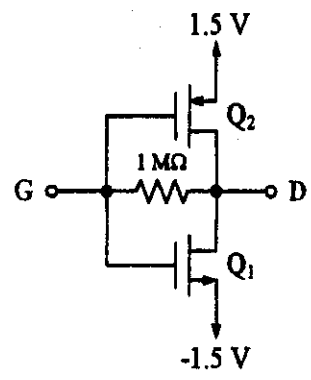


Fig. 5

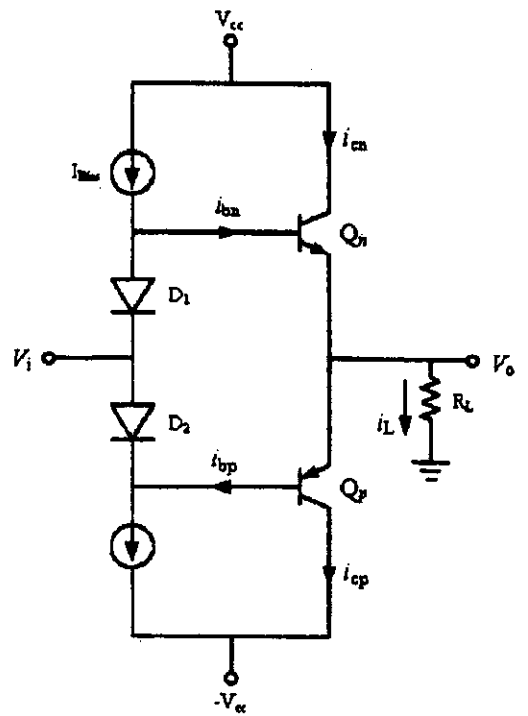


Fig. 6

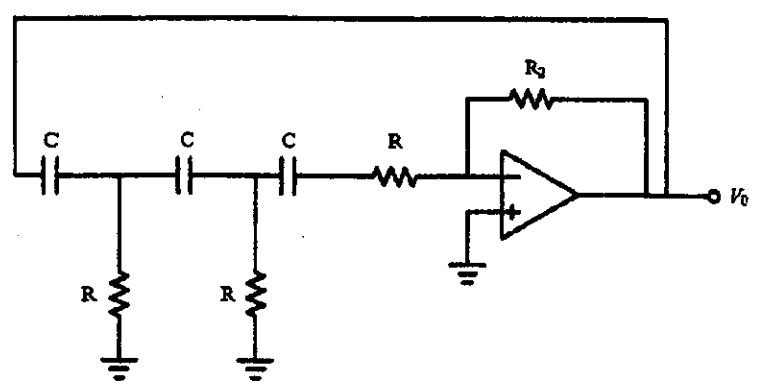


Fig. 7