

PART I:

計算機結構

1. 解釋名詞:

- (1) memory-mapped I/O (2%) (2) pipeline processing (2%)
(3) relative-addressing mode (2%) (4) RISC (1%)
(5) systolic array processor (2%) (6) shuffle-exchange network (1%)

2. (1) 何謂 cache memory? (2%)

(2) 舉出三種 main memory 至 cache memory data transformation 的 mapping types. (4%)

3. 試列舉四種 CPU 與 peripheral devices 間傳送資料 (data transfer) 的方式, 並舉例說明之. (6%)

4. (1) 何謂 daisy chain priority interrupt? (2%)

(2) 試繪出含有三個 devices 及一個 CPU 的 daisy chain priority interrupt 系統結構圖, 並詳述其中一個 stage 的 priority arrangement 電路. (4%)

5. 比較 control-driven computers, data-driven computers 及 demand-driven computers 之異同. (4%)

6. 試說明設計 firmware program 及 software program 的差異. (4%)

7. 試說明 future generation computer systems 應有的特性. (4%)

8. 試於 IBM PC 上設計一個 intelligent printer I/O card, 使能

(1) 同時控制一台具 centronic interface 及一台具 RS-232C interface 的 printers 印製檔案,

(2) 重覆印製同一檔案多次, 而僅需接受自 host 的 command 一次,

(3) 在 printers 尚未完成印製工作時, host 能執行其它工作 (如利用 PE-II 編輯另一檔案),

繪出 block diagram, 並說明各 block 的機能與動作. (5%)

9. 設有一個 computing problem, 若在 uniprocessor 執行需一單位時間 ($T_1=1$), 現利用一套 n -processor parallel computer 計算同一問題, 而且

(1) 對 n 個可能的 operating modes (在 n -processor system 中, 可能同時指定其中 i 個 processors 執行運算, $i=1, 2, \dots, n$) 選擇機率相同, 即 $f_i=1/n$,

(2) 對任一 operating mode, 其每個 working processor 的工作量相同, 即 $d_i=1/i$,

試證明此一 n -processor parallel computer 的 speedup 上界 (upper bound) 為 $n/\ln n$. (5%)

PART II:

Digital Design

- Describe the procedure for the subtraction with $(r-1)$'s complement. Assume the minuend M and the subtrahend N are in base r and both are positive. (4%)
 - Prove the above procedure. (5%)
- Using exclusive-OR (or equivalence) gates to design a combinational circuit which checks for even parity of four bits (Don't use other kinds of gates). (8%)
- Design a counter that counts the decimal digitals according to the 2,4,2,1. Use T flip-flops. (10%)
- Implementing a full-adder with two half-adders and an OR gate. (3%)
 - Design a 4 bits full-adders with look-ahead carry and compute the total delay time in this adder. (8%)
- A digital system has three registers: AR, BR, and PR. Three flip-flops provide the control functions for the system: S is a flip-flop which is enabled by an external signal to start the system's operation; F and R are used for sequencing the micro-operations. A fourth flip-flop, D, is set by the digital system when the operation is completed. The function of the system is described by the following register transfer operation:
$$\begin{aligned} S: & PR \leftarrow 0, S \leftarrow 0, D \leftarrow 0, F \leftarrow 1 \\ F: & F \leftarrow 0, \text{ if } (AR=0) \text{ then } (D \leftarrow 1), \text{ if } (AR \neq 0) \text{ then } (R \leftarrow -1) \\ R: & PR \leftarrow PR+BR, AR \leftarrow AR-1, R \leftarrow 0, F \leftarrow 1 \end{aligned}$$
 - Show that the digital system multiplies the contents of AR and BR and places the product in PR.
 - Draw a block diagram of the hardware implementation. Include a start input to set flip-flop S and a done output from flip-flop D. (12%)