

國立成功大學 79 學年度資訊工程研究所考試(計算機概論試題)

PART I. LOGIC DESIGN.

1. Design an 8421 BCD adder/subtractor with a control input to select between the addition and subtractions.
 - (a) Use logic circuit. (7%)
 - (b) Use a ROM. (3%)
2. (a) Reduce the number of states in the following state table and tabulate the reduced state table. (5%)

Present state	Next state		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	f	b	0	0
b	d	c	0	0
c	f	e	0	0
d	g	a	1	0
e	d	c	0	0
f	f	b	1	1
g	g	h	0	1
h	g	a	1	0

- (b) If the binary assignment of the reduced state table of (a) is assigned as (001, 010, 011, 100, 101, ...) from state a in order. Design the sequential circuit with three JK flip-flop. (Use A, B, C, as the FF's name). (15%)
3. A multiplier which uses the standard add and shift algorithm (fig. 1) is shown in fig. 2, the MQ-register holds the multiplier and the MPCND-register holds the multiplicand, Z_1, Z_2, Z_3, Z_4 are the control signal of control circuit.
 - (a) Draw the ASM (Algorithm State Machine) chart of the control circuit of this multiplier. (5%)
 - (b) Derive the state table for the ASM chart of (a). (5%)
 - (c) Design the control circuit with D flip-flop and a decoder. (5%)
 - (d) Draw the equivalent state diagram and design the circuit with one flip-flop per state. (5%)

BEGIN Multiplication

WAIT UNTIL start

AC: = 0; E: = 0;

REPEAT 32 times

BEGIN

IF MQ[32] = 1 THEN E AC: = AC + MPCND;
RIGHTSHIFT(E AC MQ);

END

Completion: = 1

END Multiplication

Fig. 1

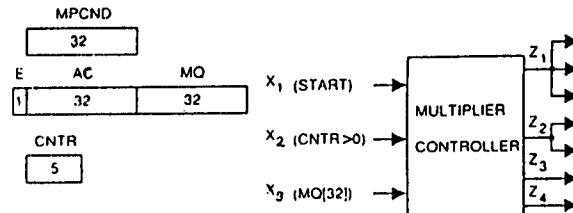


Fig. 2

134

七六、三、二、〇〇〇

(甲)

PART II.

1. 何謂 Nanoprogrammed Computer. 並說明它的優缺点。(7%)
2. 在設計 Control unit 時有所謂的 delay-element method 之設計法. 舉例說明之。(7%)
3. 試述降低 pipelined computer 中 reinitialization (resynchronization) rate 的方法。(7%)
4. 說出至少兩種增加 CPU-memory interface bandwidth 之方法。(7%)
5. Bus Arbitration 之設計方式有那幾種? 說明之。(7%)
6. 解釋名詞: (15%)
① RISC ② Silicon Compiler ③ data coherence ④ data dependency
⑤ Reentrant ⑥ SIMD ⑦ latency ⑧ starvation ⑨ ASIC
⑩ Associated memory.