

※ 考生請注意：本試題不可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. The op amplifier, shown as Fig.1, is ideal with output saturation levels of ± 12 V. Assume that when conducting the diode exhibits a constant voltage drop of 0.7 V. (a) Please find V_A , V_O and V_- for $V_I = +1$ V (6%)(b) Please find V_A , V_O and V_- for $V_I = -1$ V (6%) (c) find the average output voltage obtained when V_I is a symmetrical square wave of 1-kHz frequency, 5-V amplitude and zero average. (3%)


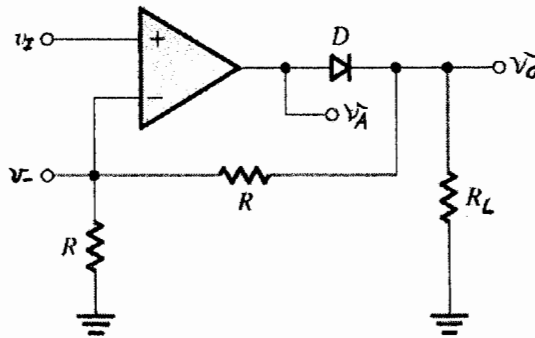


Fig. 1

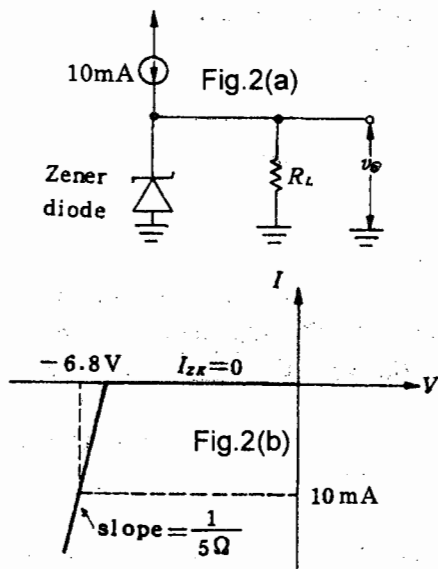2. A shunt voltage regulator consists of a Zener diode supplied by a constant current of 10 mA. At this operating current the Zener resistance is 5Ω and the Zener voltage is 6.8 V. The circuit and diode I-V characteristics are shown in Fig.2(a) and Fig.2(b), respectively. If the regulator is loaded by a resistor of $2k\Omega$, the output voltage decreased by _____ mV.(10%)



2. In the circuit of Fig. 3, the NMOS transistor has $|V_t| = 0.9$ V and $V_A = 50$ V and operates with $V_D = 2$ V. Find the $v_o/v_i =$ _____ V/V. (10%)
4. In the circuit of Fig. 4, v_{sig} is a small sine-wave signal with zero average. The transistor has $\beta = 100$. (a) When the $R_E =$ _____ Ω , the transistor has a dc emitter current of about $I_E = 0.5$ mA (5%) (b) When the $R_C =$ _____ Ω , the transistor has a dc collector voltage of about $V_C = 5$ V (5%) (c) When the $R_L = 10$ k Ω and $r_o = 200$ k Ω , the overall voltage gain $A_v = v_o/v_{sig} =$ _____ V/V. (5%)

(續下頁)

※ 考生請注意：本試題不可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

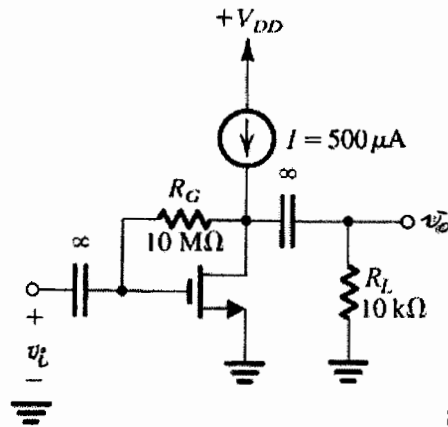


Fig.3

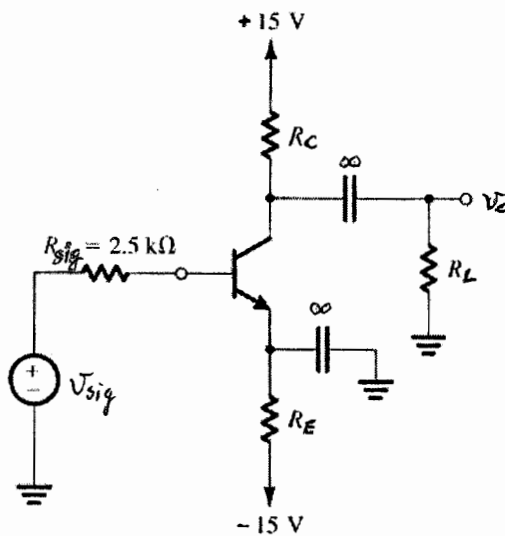


Fig.4

5. A feedback circuit is shown in Fig. 5, find (a) I_{out}/I_{in} and (b) R_{out} . Assume the transistors to have $\beta=100$ and $V_A=75$ V. (20%)

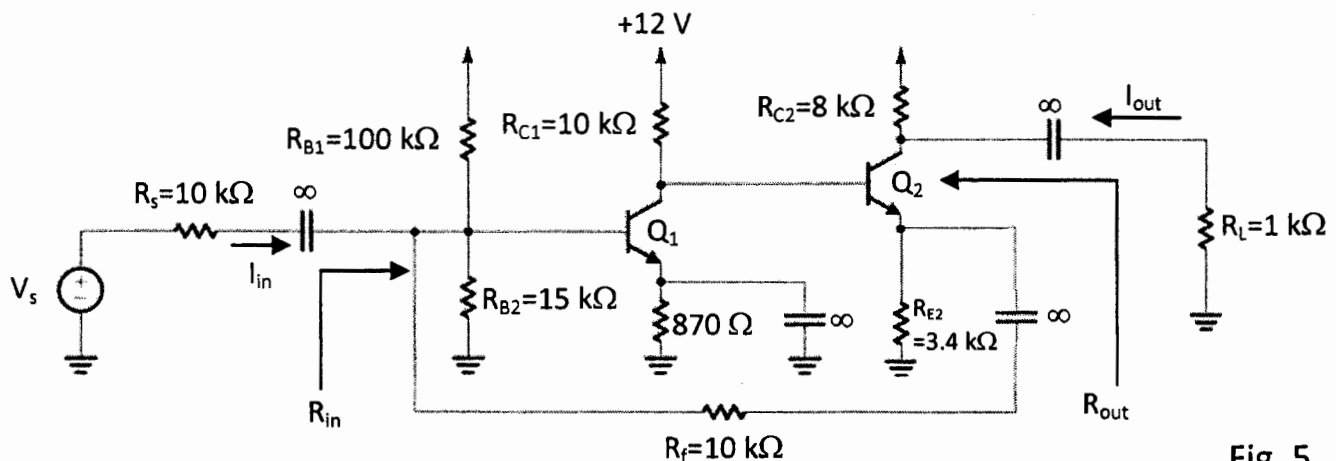


Fig. 5

(續下頁)

※ 考生請注意：本試題不可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

6. In Fig. 6, find the digital logic relationship between Y and A, B, C, and D. (15%)

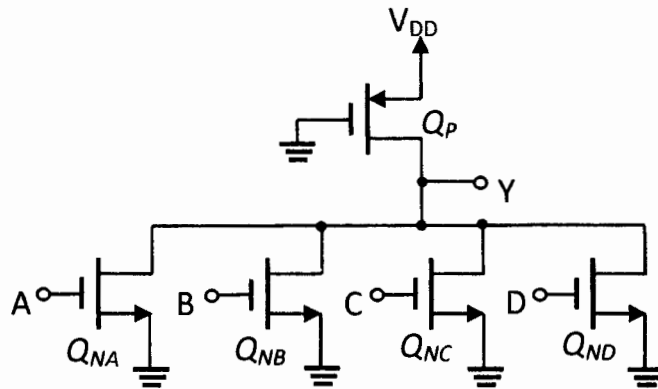


Fig. 6

7. For the circuit in Fig. 7 in which the transistors have $V_{BE}=0.7\text{ V}$ and $\beta=100$, find g_{meq} , v_o/v_i , and R_{in} . (15%)

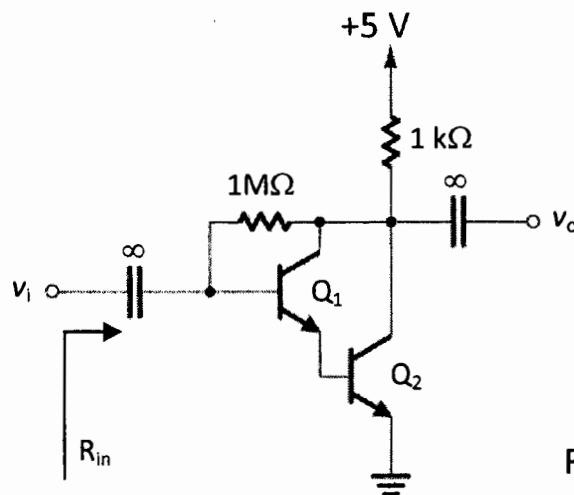


Fig. 7