

※ 考生請注意：本試題不可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. Transistor in Fig. 1 has $V_{BE(on)} = 0.7$ and $\beta = 100$. D_1 is a Schottky diode with turn on voltage of 0.3 V. D_2 is a Zener diode with $V_Z = 5.4$ V. Please find the output voltage (V_{out}) when input voltage (V_{in}) is 6 V. (10%)

 


Fig. 1

2. Consider the BiCMOS amplifier shown in Fig. 2. The BJT has $|V_{BE}| = 0.7$ V, $\beta = 200$, $C_{\mu} = 0.8$ pf, and $f_T = 600$ MHz. The NMOS transistor has $V_t = 1$ V, $K'n(W/L) = 2$ mA/V², and $C_{gs} = C_{gd} = 1$ pF. (30%)

(a) Consider the dc bias circuit. Neglect the base current of Q_2 in determining the current in Q_1 . Find the DC bias currents in Q_1 and Q_2 . Evaluate the small signal parameters of Q_1 and Q_2 at their bias points.

(b) Consider the circuit at mid-band frequencies. First determine the small signal voltage gain V_o/V_i . Then use Miller theorem on R_G to determine the amplifier input resistance R_{in} . Finally, determine the overall voltage gain V_o/V_{sig} .

(c) First consider the circuit at low frequencies. Determine the frequency of poles due to C_1 and C_2 , and hence estimate the lower 3-dB frequency, f_L . Second consider the circuit at high frequencies. Use Miller's theorem to replace R_G with a resistance at the input. Use open circuit time constants to estimate f_H .

 


Fig. 2

3. Figure 3 shows a MOS differential amplifier. (30%)

- (1) Derive I_{bias} (current flowing through M_1) in terms of R , $\mu_n C_{ox}$ and $(W/L)_n$, where $(W/L)_1 = 2(W/L)_n$, $(W/L)_2 = (W/L)_4 = (W/L)_5 = (W/L)_n$, $(W/L)_3 = 4(W/L)_n$, and $(W/L)_6 = (W/L)_7 = (W/L)_p$. Assume $|V_t|$ is the same for all devices.
- (2) Derive the small-signal voltage gain v_o/v_i .

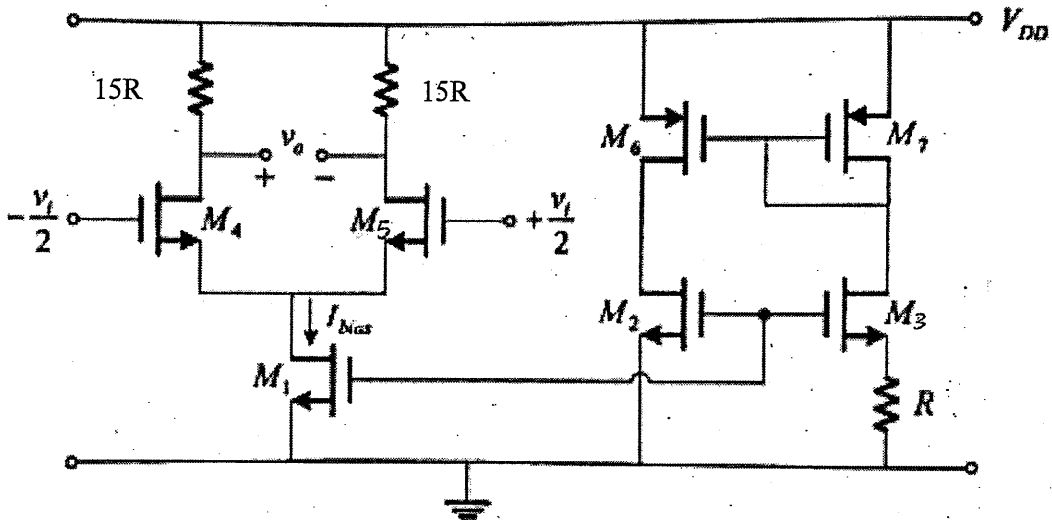


Fig. 3

4. The V_{DD} , input DC bias, and I_{BIAS} in Fig. 4 are 5 V, 3 V, and 300 μA , respectively. The transistors in Fig. 4 have $\mu_n C_{ox} W_1/L_1 = \mu_p C_{ox} W_2/L_2 = \mu_p C_{ox} W_3/L_3 = \mu_p C_{ox} W_4/L_4 = 200 \mu A/V^2$, $V_{tn} = 1$ V, and $V_{tp} = -1$ V. (20%)

- (a) What is the output DC voltage of the circuit?
- (b) Find the small-signal voltage gain of the circuit.

 


Fig. 4

5. For an ideal BJT the I_C doesn't vary with the V_{CE} when BJT is in active mode. However, each I_C - V_{CE} curve in the realistic I_C - V_{CE} characteristics of BJT of Fig. 5 shows that the I_C slightly increases with increasing the V_{CE} when BJT is in active. The injected carrier profiles in base region of BJT with different scenarios of bias are showing in Fig. 6. Which figure in Fig. 6 is the cause of slight increases of I_C with enlarged V_{CE} for BJT in active mode? And give your interpretation about the figure you pick in Fig. 6 why it is the cause of slight increases of I_C with enlarged V_{CE} for BJT in active mode. (10%)

 


Fig. 5

 


Fig. 6