 


※ 考生請注意：本試題 可 不可 使用計算機

1. For the amplifier in the Fig. 1, let the parameters of transistors M_1 , M_2 and Q_1 $\mu_n C_{ox} = 200 \mu A/V^2$, $V_t = 1V$, $(W/L)_{M1} = 10$, $(W/L)_{M2} = 20$ and $\beta(Q_1) = 499$. Please find
- Output DC voltage v_o (10%)
 - Small signal voltage gain v_o/v_i . (10%)

Fig. 1



2. The differential amplifier circuit of Fig. 2 utilizes a resistor connected to the negative power supply to establish the bias current I , where Q_1 and $Q_2 \alpha \sim 1$
- For $v_{B1} = v_{id}/2$ and $v_{B2} = -v_{id}/2$ where v_{id} is a small signal with zero average, find the magnitude of the differential gain, $|v_o/v_{id}|$ (5%)
 - For $v_{B1} = v_{B2} = v_{icm}$, find the magnitude of the common-mode gain, $|v_o/v_{icm}|$. (5%)
 - Find the CMRR. (5%)

 


Fig. 2


(背面仍有題目,請繼續作答)

※ 考生請注意：本試題 可 不可 使用計算機

3. The circuit shown in fig. 3 is intended to supply a voltage to floating loads while making greatest possible use of the available power supply.

- (a) Assuming ideal OP amps, sketch the voltage waveforms at nodes B and C for a 1-V peak-to-peak sine wave applied at node A. Also sketch the v_o . (5%)
- (b) What is the voltage gain v_o/v_i . (5%)
- (c) Assuming that the OP amps operate from ± 15 -V power supplies and that their output saturates at ± 14 V. What is the largest sine wave output that can be accommodated? Specify both its peak to peak and rms values. (5%)

Fig. 3

 

4. For the circuits in Fig. 4, $\mu_n C_{ox} = 2.5 \mu_p C_{ox} = 20 \mu A/V^2$, $|V_t| = 1V$, $\lambda = 0$, $\gamma = 0$, $L = 10 \mu m$, and $W = 30 \mu m$, unless otherwise specified. Find the labeled currents and voltages. (15%)

 


Fig. 4

系所組別： 光電科學與工程研究所

考試科目： 電子學

考試日期： 0307，節次： 1

※ 考生請注意：本試題 可 不可 使用計算機

5. For a digital logic inverter fabricated in a 0.8- μm CMOS technology for which $k_n' = 120 \mu\text{A}/\text{V}^2$, $k_p' = 60 \mu\text{A}/\text{V}^2$, $V_{tn} = |V_{tp}| = 0.7 \text{ V}$, $V_{DD} = 3 \text{ V}$, $L_n = L_p = 0.8 \mu\text{m}$, $W_n = 1.2 \mu\text{m}$, and $W_p = 2.4 \mu\text{m}$, find:

- (a) the output resistance for $v_O = V_{OL}$, and for $v_O = V_{OH}$ (5%)
- (b) the maximum current that the inverter can sink or source while the output remains within 0.1 V of ground or V_{DD} , respectively (5%)
- (c) V_{IH} , V_{IL} , and noise margins NM_H , NM_L (5%)
- (d) the peak current drawn from the 3-V supply during switching (5%)

6. For the transistor shown in Fig. 5, assume $\alpha=1$ and $v_{BE} = 0.5 \text{ V}$ at the edge of conduction. What are the values of V_E and V_D for $V_B = 0\text{V}$? For what value of V_B does the transistor cut off? Saturate? In each case, what values of V_E and V_C result? (15%)

 


Fig. 5